

Registration No. :

--	--	--	--	--	--	--	--	--	--

Total number of printed pages – 3

B. Tech
BEES 2211

Third Semester (Back/Special) Examination – 2013

NETWORK THEORY

BRANCH : AEIE, CSE, EC, EEE, EIE, ELECTRICAL, ETC, IEE, IT

QUESTION CODE : D224

Full Marks – 70

Time : 3 Hours


Answer Question No. 1 which are compulsory and any **five** from the rest.
The figures in the right-hand margin indicate marks.

1. Answer the following questions : 2×10
- (a) What is meant by linear and nonlinear elements ?
- (b) Explain how voltage source with a source resistance can be converted into an equivalent current source.
- (c) In three-phase circuit, what do you mean by balanced load ?
- (d) Mention the Properties of a parallel RLC circuit.
- (e) Represent graphically for the expression $y = u(a - t)$.
- (f) Give the limitations of using superposition theorem.
- (g) Why transients occur in electric circuits ?
- (h) What is Routh-Hurwitz stability criterion ?
- (i) What is cut set matrix ? Explain in brief.
- (j) Define Laplace transform. Find L.T. of $e^{-at} \sin(\omega t)$.
2. (a) Find the Z-parameter for the network. The network is a T-type network. Series branches are $5\text{ k}\Omega$ and $3\text{ k}\Omega$, The shunt branch being 12Ω . 5

P.T.O.


(b) Explain and derive the relationships for bandwidth and half power frequencies of RLC series circuit. 5

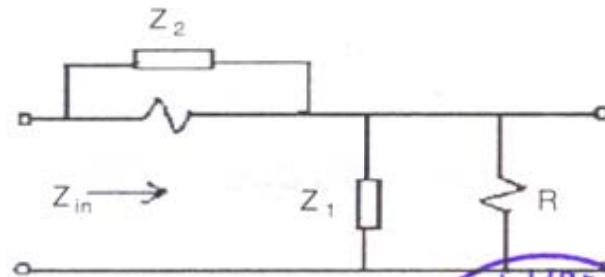3. (a) Determine the conditions under which the input impedance of the network shown in figure will be equal to R. 5




(b) Draw and explain the characteristics of ideal band-pass and band-stop filter. 5

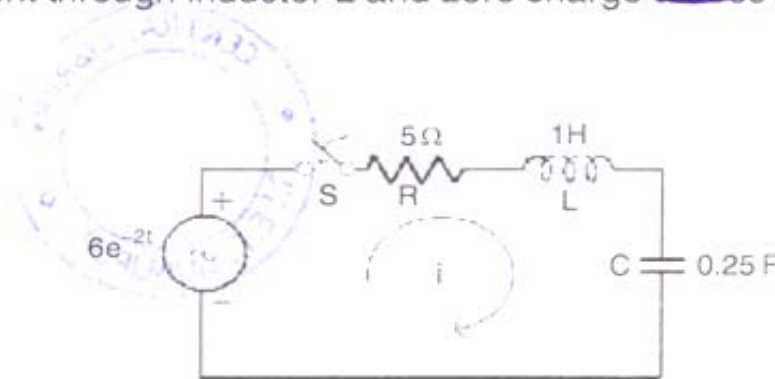4. In the circuit shown in figure, the switch is closed at time $t=0$. Obtain $i(t)$. Assume zero current through inductor L and zero charge across C before closing the switch. 10




5. (a) A 2-port network has equations $V_1 = 4I_1 + I_2$ and $V_2 = 3I_1 + 3I_2$. Determine its ABCD parameters. 5

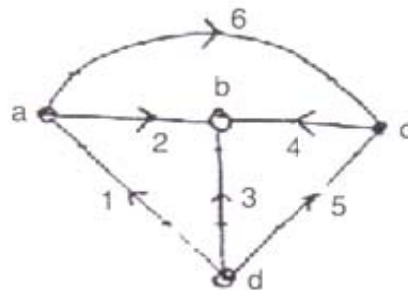
(b) For the graph shown in the figure, find the complete incidence matrix. 5



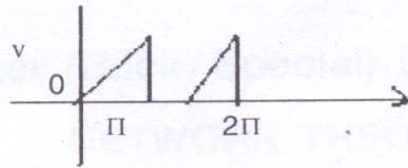6. (a) Find the trigonometric Fourier series for the wave shown in figure and plot the spectrum. 5



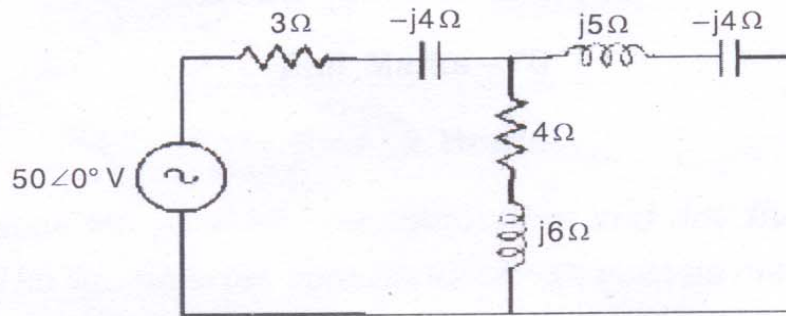- (b) Determine the Thevenin's equivalent for the figure. 5



7. (a) What are ABCD parameters? Prove that $AD - BC = 1$. 5
 (b) Explain with example, odd symmetry and even symmetry of Periodic waveforms. 5
8. Write short notes on any two 5×2

- (a) Network synthesis
 (b) Laplace Transform
 (c) Bandwidth and Q-factor
 (d) Phase sequence.

