

Registration No. :

--	--	--	--	--	--	--	--	--	--

Total number of printed pages – 3

B. Tech
BEES 2211

Third Semester Examination – 2013

NETWORK THEORY

BRANCH : EIE, IT, CSE, EC, ETC, EEE, IEE, ELECTRICAL, AEIE

QUESTION CODE : C- 506

Full Marks – 70

Time : 3 Hours

Answer Question No. 1 which is compulsory and any **five** from the rest.
The figures in the right-hand margin indicate marks.


1. Answer the following questions :

2×10

- Explain why the voltage across a capacitor cannot change instantaneously.
- Explain how voltage source with a source resistance can be converted into an equivalent current source.
- Name the four different types of dependent sources in electric circuits.
- A voltage source has internal impedance $(10 + j15)$ ohm. Find the load impedance for maximum power transfer.
- Write the formula to find the maximum output voltage in single and double tuned circuits.
- What are critical frequencies ? Why they are so called ?
- Distinguish between steady state and transient response.
- List any two advantages of 3-phase system over 1-phase system.
- Write the relation between the line and phase value of voltage and current in a balanced star connected load.
- What is meant by Unilateral and Bilateral element ?

P.T.O.

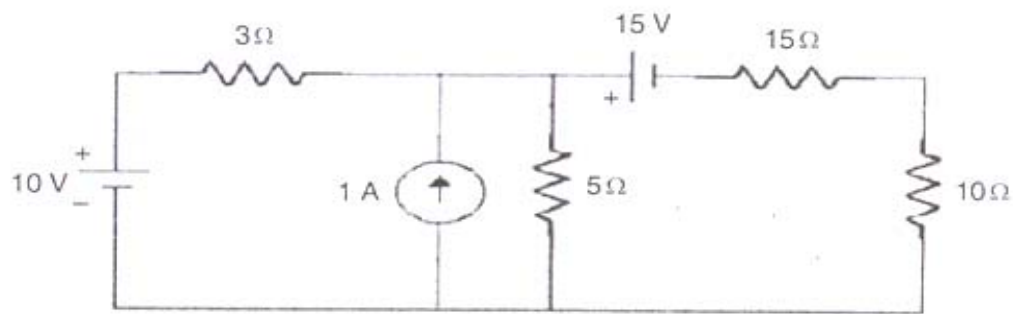2. (a) Find the power dissipated in 10 ohm resistor for the circuit shown in figure. 5




- (b) The transform voltage $V(s)$ of a network is given by $V(s) = \frac{4s}{(s+2)(s^2+2s+2)}$ plot its pole-zero diagram and hence obtain $v(t)$. 5


3. (a) A pure resistor, a pure capacitor and a pure inductor are connected in parallel across a 50Hz supply, find the impedance of the circuit as seen by the supply. Also find the resonant frequency. 5

- (b) A three-phase delta connected load has $Z_{ab} = (100 + j0)$ ohms, $Z_{bc} = (-j100)$ ohms and $Z_{ca} = (70.7 + j70.7)$ ohms is connected to a balanced 3-phase 400 V supply. Determine the line currents I_a , I_b and I_c . Assume the phase sequence abc. 5

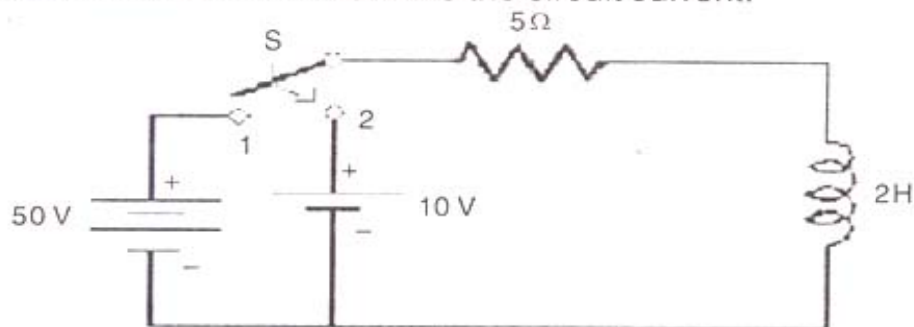
4. In the circuit shown in figure, switch S is in position 1 for a long time and brought to position 2 at time $t = 0$. Determine the circuit current. 10



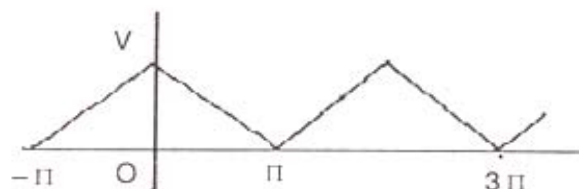5. (a) Find the trigonometric Fourier series for the triangular wave shown in fig. and plot the spectrum. 5



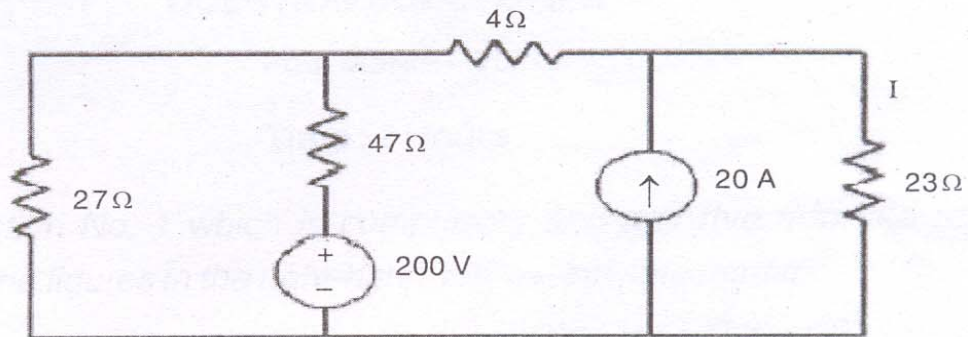- (b) When connected to a 230 V, 50 Hz single-phase supply, a coil takes 50 kVA and 45 kVAR. For this coil calculate resistance, inductance of coil and power consumed. 5
6. (a) An alternating current is expressed as $i = 14.14 \sin 314t$. Determine rms current, frequency and instantaneous current when $t = 0.02$ ms. 5
- (b) What is phase sequence ? Explain its significance. 5
7. (a) Compute the current in 23 ohm resistor using superposition theorem for the circuit shown below. 5



- (b) A balanced 3-phase Delta connected load with voltage of 200 V, has line currents as $I_1 = 10 \angle 90^\circ$, $I_2 = 10 \angle -150^\circ$ and $I_3 = 10 \angle -30^\circ$
- (i) What is the phase sequence ?
- (ii) What are the impedances ? 5
8. Write short notes on any **two** : 5×2
- (a) Norton's theorem
- (b) Driving point impedance
- (c) Time constant
- (d) Quality factor

