

Registration No. :

--	--	--	--	--	--	--	--	--	--

Total number of printed pages – 3

B. Tech
PCEC4201

Third Semester (Back/Special) Examination – 2013

ANALOG ELECTRONICS CIRCUITS

BRANCH : AEIE, BIOMED, CSE, EC, EEE, ELECTRICAL, ETC, IEE, IT

QUESTION CODE : D 217

Full Marks – 70

Time : 3 Hours

Answer Question No. 1 which is compulsory and any **five** from the rest.

The figures in the right-hand margin indicate marks.

1. Answer the following questions :

2 × 10

- What is dynamic resistance of a diode? How it is evaluated numerically?
- Three OPAMP based instrumentation amplifiers are better than single OPAMP based instrumentation amplifiers. Justify.
- How does base resistor (R_B) affect the input resistance of a CE amplifier? Justify
- What are the small signal h-parameters that are determined from input characteristics of a transistor amplifier?
- Why wein bridge oscillators are most popular in audio frequency range?
- What are two salient features of a 'buffer amplifier'?
- What is the bandwidth of the amplifier when the rise time is 0.1 msec? What should be the rise time of an ideal voltage amplifier?
- What is CMRR of an OPAMP? How CMRR can be increased during the manufacturing of OPAMP?

P.T.O.

- (i) What is pinch-off voltage of FET ? Why drain current is almost constant when source-drain voltage exceeds pinch-off voltage ?
- (j) Why a constant current source is used in place of R_E in the differential amplifier stage of the OPAMP ?
2. (a) Draw a self bias circuit of transistor amplifier. Then, find the load line and operating point (I_{CQ} , V_{CEQ}) of the above transistor amplifier in terms of its circuit components. 5
- (b) Derive an expression for the overall bandwidth when N no. of identical voltage amplifiers is connected in cascade. 5
3. (a) Explain the odd harmonic cancellation property of a push pull power amplifier. Justify your answer mathematically. 5
- (b) Explain the principle operation of a push pull power amplifier. Compare its performance with Complementary symmetry power amplifier. 5
4. (a) Derive the condition for oscillation in RC phase shift oscillator. 5
- (b) Derive the input impedance (Z_i) and output impedance (Z_o) of a unit feedback voltage series-ve feedback amplifier in terms of its open loop parameters. 5
5. (a) Draw a voltage divider bias emitter follower circuit. Draw its r_e equivalent circuit. Derive its voltage gain. What is its importance in analog circuits ? 5
- (b) Design a 1st order active low pass filter which have gain = 5 and cut-off frequency 5 KHz. Suggest, how the bandwidth of the can be improved without increasing the rise time of the circuit. 5
6. (a) A FET amplifier in common-source configuration uses a load resistance of $250\text{ K}\Omega$. The ac drain resistance of the device is $100\text{ K}\Omega$ and the transconductance is 0.5 mA/V . Calculate the voltage gain and the output resistance of the amplifier. 5

(b) The voltage gain of a transistor amplifier is 50. Its input and resistances are $1\text{ K}\Omega$ and $40\text{ K}\Omega$. If the amplifier is provided with 10% negative voltage feedback in series with the input, calculate the closed loop voltage gain, input resistance and output resistance. 5

7. (a) Draw a three OPAMP based instrumentation amplifier circuits and Derive its voltage gain in terms of circuit components. Mention its applications. 5

(b) Design a OPAMP based analog circuits which will give an output voltage, $V_0 = 0.5 V_1 - 2 V_2 + 0.25 V_3$, Where, V_1 , V_2 and V_3 are three input voltages. 5

8. Write short notes on any **two** of the following: 5×2

(a) Stability of transistor Biasing

(b) Cascode amplifiers

(c) Current mirror circuit

(d) Miller effect capacitance.