

Registration No. :

--	--	--	--	--	--	--	--	--	--

Total number of printed pages – 3

B. Tech
PCEC 4201

Third Semester Examination – 2012-13

ANALOGUE ELECTRONICS CIRCUIT

Full Marks – 70

Time : 3 Hours

*Answer Question No. 1 which is compulsory and any **five** from the rest.*

The figures in the right-hand margin indicate marks.

1. Answer the following questions : 2×10
- (a) Cite two operational differences between a MOSFET and an FET.
 - (b) State the input impedance of a CC stage in terms of the hybrid parameters. What is its significance ?
 - (c) What is a current buffer ? Where is it used ?
 - (d) What happens to the overall bandwidth when 10 identical amplifiers are cascaded. Why ?
 - (e) Explain how dc load line is different from ac load line. Write two viewpoints.
 - (f) Which switch is faster ? A BJT or a MOSFET ? Justify.
 - (g) Write the use(s) of CMOS. Draw one such circuit.
 - (h) Explain how do you determine the hybrid input parameters of a BJT graphically.
 - (i) Why bias stabilization is important ? State at least two reasons.
 - (j) How does an emitter resistance affect the frequency response of a CE amplifier ? Illustrate.

P.T.O.

2. (a) Under what conditions does a MOSFET behave as a linear resistor? Hence, derive an expression for the resistance offered by the device under this condition. Show your steps clearly along with the underlying assumption(s). 5
- (b) An E-type NMOS transistor with a threshold voltage of 0.7 V has its source grounded and the gate is connected to 1.5 V. In what region does the device operate for
- (a) $V_D = 0.6$ V,
 (b) $V_D = 0.8$ V and
 (c) $V_D = 3.3$ V?
- Hence find the current in each case for $\mu_n C_{ox} = 100 \frac{\mu A}{V^2}$, and $W = 10 \mu m$ and $L = 1 \mu m$. 5
3. (a) Derive an expression for the upper 3-dB cut off frequency for a CE amplifier. State your assumptions clearly. 5
- (b) An NPN Si transistor with grounded emitter with $V_{BE} = 0.7$ V is operated with a collector current of 1 mA. A 10 K Ω resistor connects the collector to a 12 V supply. What is V_{CE} ? Now, if a signal is applied to the base raises v_{BE} to 705 mV, find the resulting total collector current i_C and the total collector voltage v_C . For this situation, what are v_{be} and v_c ? 5
4. (a) In a certain MOSFET amplifier using voltage divider biasing, we need to have a dc drain current of 0.5 mA. The MOSFET has a threshold voltage of 1 V and $k'_n \frac{W}{L}$ of $1 \frac{mA}{V^2}$. Use a power supply of 12 V. Design a suitable circuit. Draw your final circuit along with the components. 5
- (b) Derive an expression for the voltage gain of a CS amplifier having a drain resistance R_D and a source resistance R_S . Draw the small signal equivalent circuit. 5

5. (a) Derive the frequency of oscillation in a phase shift oscillator. Draw the small-signal equivalent circuit. 5
- (b) Derive suitable expressions for the input resistance and the voltage gain of a transconductance amplifier that uses negative feedback. 5
6. (a) Derive the expressions for the differential gain and the common-mode gain of a differential amplifier with the help of the respective small signal equivalent circuits. 5
- (b) Discuss an instrumentation amplifier. Where is it used? 5
7. (a) Derive the conversion efficiency of a class-B power amplifier. 5
- (b) Discuss the circuit operation of a class-A power amplifier. 5
8. (a) Design a suitable circuit for furnishing a reference bias current of 0.43 mA to $\mu A 741$. Use power supplies of ± 12 V. You may assume other parameters in a suitable manner. 5
- (b) To what feedback topology, the non-inverting amplifier does belong? Hence derive an expression for its voltage gain and output impedance? 5
-