

Registration No. :

--	--	--	--	--	--	--	--	--	--

Total number of printed pages – 7

B. Tech

PCEC 4201(N)/CPES 5202(O)

Third Semester Examination – 2010

ANALOGUE ELECTRONICS CIRCUITS (New and Old Course)

Full Marks – 70

Time : 3 Hours

(Students are required to give their answer any one Course according to the Syllabus)

(NEW COURSE)

Answer Question No. 1 which is compulsory and any five from the rest.

The figures in the right-hand margin indicate marks.

1. Answer in brief all the following questions : 2×10
- What is the need of a CMOS circuit? Draw a basic CMOS circuit.
 - Compare fixed bias and self bias of BJT circuits from two points of view.
 - Prove that a FET is a voltage controlled device.
 - What do you mean by small-signal analysis? How small is small?
 - What is the need of a current-mirror? Draw one circuit.
 - What is base-width modulation? What is its effect?
 - Draw the equivalent circuit of a CE amplifier using Miller effect. What is the upper 3-dB frequency of such a single-pole circuit?
 - What is the transfer function of a CE amplifier at low frequencies? Give the location of its poles and zeros.

P.T.O.


- (i) What is frequency distortion ? Why does it take place ?
- (j) What is a virtual ground ? What is its effect on an op-amp operation.
2. (a) For any single-transistor amplifier prove that $R_i = \frac{h_i}{1-h_r A_v}$. 5
- (b) Consider an emitter follower and show that as the emitter resistance $R_e \rightarrow \infty$ $R_i \rightarrow h_{ie} + \frac{1+h_{fe}}{h_{oe}} \approx \frac{1}{h_{oe}}$. 5
3. (a) Show that the transconductance g_m of a JFET is related to the drain current I_{DS} given by $g_m = \frac{2}{|V_P|} \sqrt{I_{DSS} I_{DS}}$, where the symbols have their usual meanings. 5
- (b) Do you get any junction in a JFET ? Why ? 2
- (c) Draw the equivalent model of a voltage-divider biased JFET circuit under small signal conditions. 3
4. (a) Derive expressions for the stability factors of a voltage-divider biased CE amplifier. 6
- (b) Derive the input resistance of a Darlington configuration. What is its utility? 4
5. (a) Derive an expression for the 3-dB frequency f_H for a transistor at high frequencies. 5
- (b) What is gain-bandwidth product ? Hence derive an expression for f_T . 5
6. (a) What is the maximum efficiency of a class A power amplifier? Derive this. Do you really achieve this efficiency ? Why? 1+3+1+1
- (b) Prove that a class B power amplifier is better than a class A power amplifier. 4

7. (a) Derive an expression for the voltage gain of an instrumentation amplifier. What are its applications? 4+1
- (b) Verify that the differential gain of an operational amplifier A_d is $\frac{1}{2} g_m R_c$ under the assumption of $R_s \ll h_{ie}$ and $r_{bb'} \ll r_{b'e}$. 5
8. (a) Derive the frequency of oscillation in a phase shift oscillator. How the phase shift is realized? 4+1
- (b) What happens to the input resistance of a transconductance amplifier with feedback? Investigate. What kind of feedback is used here? 4+1

(OLD COURSE)


Answer Question No. 1 which is compulsory and any **five** from the rest.

The figures in the right-hand margin indicate marks.

1. Answer in  all the following questions : 2×10
- (a) Show how small signal low frequency h-parameters h_{11} , h_{12} , h_{21} , h_{22} can be graphically determined from V-I characteristics of transistor.
 - (b) Draw the r_e equivalent circuit for Emitter follower configuration of BJT and write the expression for voltage gain.
 - (c) Draw the circuit diagram for a Darlington configuration. Find the β of the configuration when $\beta_1 = 80$ and $\beta_2 = 100$.
 - (d) Explain why square wave testing is required in amplifiers.
 - (e) Explain how g_m is determined graphically in a JFET.
 - (f) What is Barkhausen criterion for oscillation ?
 - (g) What is miller effect ? Write the expression for miller effect input capacitance.
 - (h) What do you mean by CMRR ? How it affects the performance of Op-Amp ?
 - (i) What are the advantages of voltage series feedback ?
 - (j) What do you mean by distortion in a power amplifier ? Which power amplifier gives least amount of distortion ?

2. (a) Calculate V_C , V_B for the following BJT biasing circuit.

6

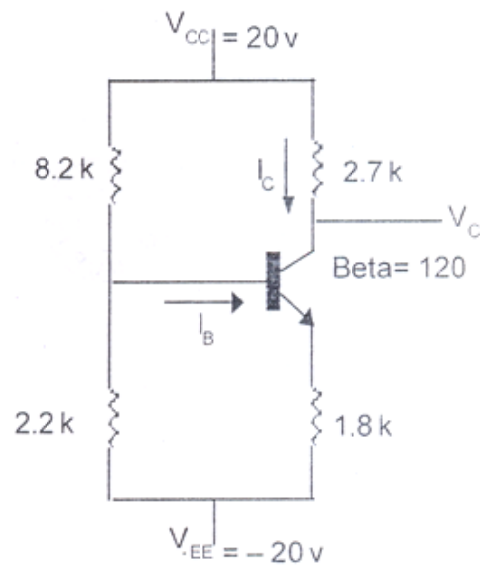


(b) Derive the voltage gain for a Common Base configuration using its r_e equivalent circuit.


4

3. (a) For the following network draw the AC equivalent circuit and derive the expression for Voltage gain, input impedance and output impedance.

6

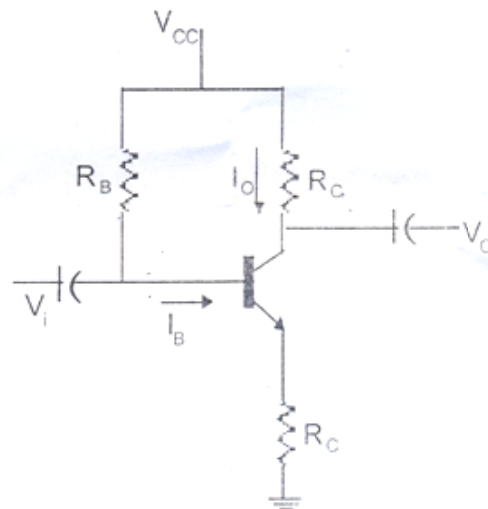

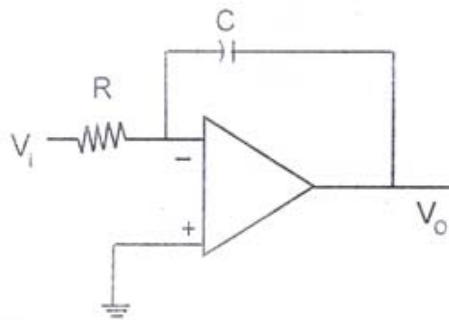- (b) Explain Frequency response of a JFET. 4
4. (a) Explain how operating is selected in a Self Bias configuration of JFET. 5
- (b) Draw the Cascode configuration and explain its operation. 5
5. (a) Draw the Op-Amp phase shift Oscillator and derive the expression for frequency of Oscillation. 5
- (b) Explain different DC offset parameters and frequency parameters of a Practical Op-Amp. 5
6. (a) For the Voltage-series feedback configuration, findout the expression for voltage gain, input impedance, output impedance. 6
- (b) Find the expression for output voltage for the following configuration : 4



7. (a) For a class B power amplifier using a supply of $V_{CC} = 30\text{v}$ and driving a load of 16 ohm. Determine the maximum input power, Output power and transistor dissipation. 6
- (b) Draw the circuit diagram of a transform coupled class-A amplifier and explain its operation. 4

8. (a) Explain how Op-Amp can be used for voltage summing application. 5
- (b) Derive the efficiency of Series-Fed class A Amplifier. 5