

Registration No :

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 02

B.Tech
PEN2B101

2nd Semester Back Examination 2018-19

ELECTRICAL & ELECTRONICS ENGINEERING

BRANCH : AEIE, AERO, AUTO, BIOTECH, CHEM, CIVIL, CSE, ECE,
EEE, EIE, ELECTRICAL, ETC, IT, MANUTECH, MECH, METTA,
MINERAL, MINING, MME, PE, PLASTIC, PT, TEXTILE

Max Marks : 100

Time : 3 Hours

Q.CODE : F1012

Answer Question No.1 (Part-1) which is compulsory, any eight from Part-II and any two from Part-III.

The figures in the right-hand margin indicate marks.

Part- I

Q1 Only Short Answer Type Questions (Answer All-10)

(2 x 10)


- What are the internal resistances of an ideal (i) 10V voltage source and (ii) 7.5A current source?
- What is duality principle? Give two examples.
- What is the relation between the line voltage and phase voltage of a 3-phase delta connection circuit?
- How diode can be used as a linear element in a circuit?
- What is slew rate of an op-amp?
- Draw the energy band diagram of a n-type semiconductor
- What do you mean by 'ratio correction factor' in an Instrument Transformer?
- Find the percentage of error for a reading of 25 mA of an ammeter provided the ammeter range is 0-50mA has an error of 2%.
- Find the resolution of a voltmeter for a voltage measurement of $4\frac{1}{2}$ digits.
- What is the semiconductor material used for the LED and how the different colors are obtained?

Part- II

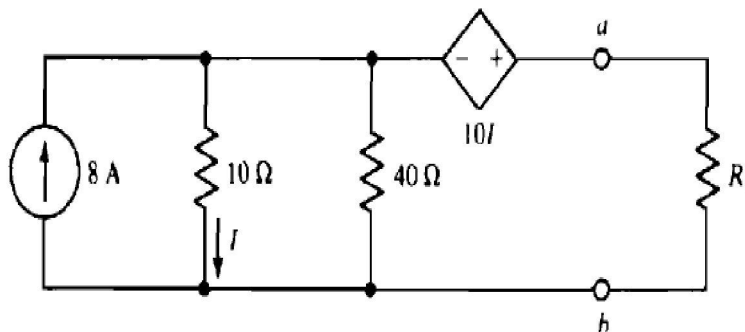Q2 Only Focused-Short Answer Type Questions- (Answer Any Eight out of Twelve)


(6 x 8)

- For the circuit given below what is the value of R_L for which maximum power transfer will be there and how much?



- Draw the simplified hybrid π model of a common emitter configuration of BJT and find out the different h-parameters.

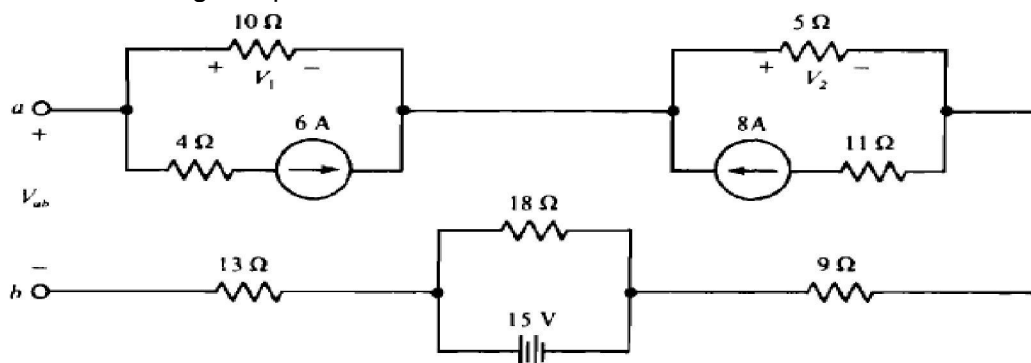- c) Determine the voltage drop across terminals a and b




- d) A PMMC instrument has a coil of dimension 10mm X 8mm. The flux density in airgap is $1 \times 10^{-3} \text{ wb/m}^2$ and spring constant is $0.3 \times 10^{-16} \text{ N-m/rad}$. Determine the number of turns required to produce angular deflection of 45° when 4A current is flowing through the coil.
- e) Prove that (i) $A + AB = A$ (ii) $A + \overline{A}B = A + B$
- f) Minimize the following expression using Boolean Algebra
 $F(A,B,C,D) = \sum (1,3,4,6,7,10,11,12,14)$
- g) What is the working principle of a current transformer? Draw and explain its phasor diagram.
- h) Realize a full adder using half adders with truth table.
- i) Explain the working of Single-phase transformer.
- j) Discuss briefly about the Magnetic materials and B-H curves.
- k) How the 3-phase power is measured by 3 wattmeter method?
- l) Draw the diagram of Instrumentation amplifier and explain its working.

Part-III

Only Long Answer Type Questions (Answer Any Two out of Four)

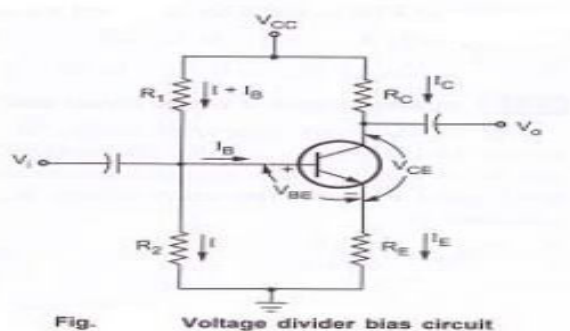- Q3 For the circuit given below $R_1 = 39 \text{ K}\Omega$, $R_2 = 6.8 \text{ K}\Omega$, $R_C = 5.6 \text{ K}\Omega$, $R_E = 1.2 \text{ K}\Omega$, $V_{CC} = 12 \text{ V}$, $\beta = 120$. Find the I_{BQ} , I_{CQ} , I_{EQ} , V_{CEQ} , V_{BQ} , V_{CQ} , and V_{BC} . (16)



- Q4 Draw the phase voltage and line voltage phasor diagram of a 3-phase delta connected balanced system. A 3 phase 230V load with a power factor of 0.5. Two wattmeters are connected to measure the power showing the input to be 7KW. Find the rating of each wattmeter. (16)
- Q5 Discuss the special diodes. (16)
- Q6 Derive the expression for the impulse response and step response of a second order circuit. (16)