

Registration No :

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 02

B.Tech  
BE2102


**2<sup>nd</sup> Semester Back Examination 2018-19**  
**BASIC ELECTRICAL ENGINEERING**  
**BRANCH : CHEM, CIVIL, CSE, ECE, EEE,**  
**ELECTRICAL, IT, MECH, PLASTIC, TEXTILE**  
**Time : 3 Hours**  
**Max Marks : 70**  
**Q.CODE : F115**

**Answer Question No.1 which is compulsory and any FIVE from the rest.**  
**The figures in the right hand margin indicate marks.**

**Q1 Answer the following questions : (2 x 10)**


- If a conductor of resistance R connected to a voltage source will compress to half of its length what will be the variation of current flowing through the conductor?
- Specify different active and passive elements with symbolic representation.
- State KCL and KVL.
- What is permeability?
- Define RMS value. How it is related to Peak factor?
- Which instruments are used for measurement of Power and Energy?
- Write the advantage of dynamometer type instruments over MI instruments.
- Why the efficiency of transformer is high among all electrical Machine and device.
- Convert  $\frac{5+j20}{3-j15}$  to polar form.
- What are the different non-conventional sources of energy?

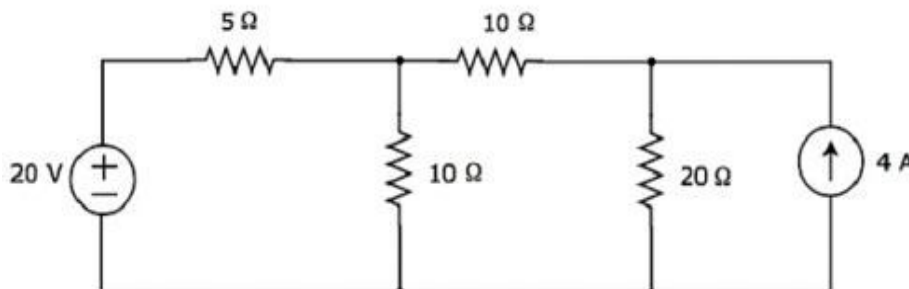- Q2**
- State and explain superposition theorem? (5)
  - Find the current flowing through 20  $\Omega$  resistor of the following circuit using superposition theorem. (5)




- Q3**
- Explain the conversion process of star network to a delta network. (5)
  - A magnetic material produces a flux density of  $10\text{wb}/\text{m}^2$  due to certain mmf. For the same mmf value, another magnetic material produces a flux density of  $12\text{wb}/\text{m}^2$ . What is the ratio of their relative permeability? (5)

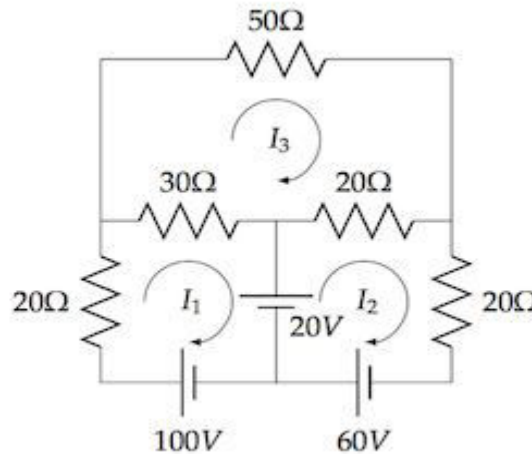- Q4** a) Derive the expression for EMF equation of transformer. (5)  
b) Find the value of  $I_1$ ,  $I_2$  and  $I_3$  by using mesh analysis. (5)



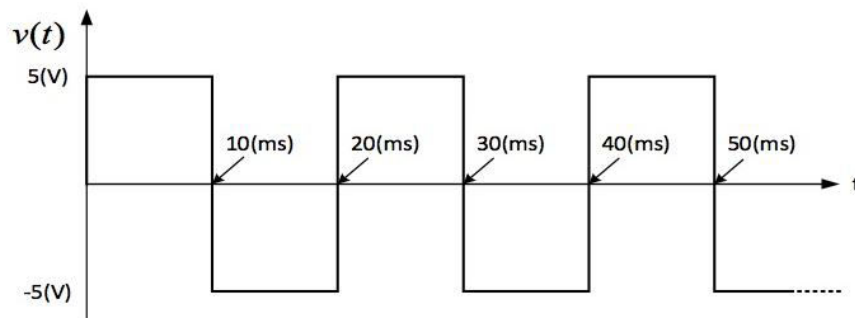- Q5** a) Find the RMS value of the voltage wave form. (5)



- b) Compare between three phase and single phase AC system. (5)

- Q6** Contrast brief idea about various generating plants. (10)

- Q7** Describe B-H curve for magnetic materials and discuss the various losses occur in the core of electrical equipment due to periodic reversal of magnetization. (10)

- Q8** Write short answer on any TWO : (5 x 2)

- Induction Motor
- Principle of operation of D.C Generator
- Transients in R-L and R-C circuit