

Registration No :

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 02

B.Tech
15BE2101

2nd Semester Back Examination 2018-19

BASICS OF ELECTRONICS

BRANCH : AEIE, AUTO, CHEM, CIVIL, CSE,
ECE, EEE, ELECTRICAL, ETC, FAT, IT, MECH, MINERAL, MINING

Max Marks : 100

Time : 3 Hours

Q.CODE : F715

Answer Question No.1 (Part-1) which is compulsory, any EIGHT from Part-II and any TWO from Part-III.

The figures in the right hand margin indicate marks.

Part- I

Q1 Only Short Answer Type Questions (Answer All-10) (2 x 10)

- What do you mean by frequency spectrum? Calculate the frequency and time period of the given sinusoidal signal. $f(t) = 5 \sin(300t)$.
- State the characteristics of an ideal Op-Amp.
- What do you mean by thermal runaway of a transistor?
- What are the advantages of negative feedback amplifier?
- What is ripple factor? Also mention its value for Full-Wave rectifier.
- Realize Ex-OR gate with four NAND gates.
- Convert $(10.01)_{10}$ to its equivalent binary number.
- Why time-base is used in Cathode Ray Oscilloscope?
- What is Q-point and load line in transistor output characteristics?
- Differentiate between Zener diode and rectifying diode.

Part- II

Q2 Only Focused-Short Answer Type Questions- (Answer Any Eight out of Twelve) (6 x 8)

- A crystal diode having an internal resistance $r_f = 20\Omega$ is used for a full wave rectification. If the applied voltage is $V = 50 \sin 2t$ and the load resistance is $R_L = 800\Omega$, determine the following :
 - I_m, I_{dc}, I_{rms} of the output
 - AC power input and power output
 - Ripple factor
- Explain how Op-Amp can be used as a summing amplifier with a neat diagram.
- Draw the circuit diagram of a common base PNP transistor configuration with its input and output characteristics.
- Why biasing circuits are required for a transistor? Discuss different biasing techniques.
- What is a differential amplifier? Derive an output voltage expression for the differential amplifier with a neat sketch.
- Which logical gates are considered as universal gates? Draw the circuit diagrams showing the universal properties of any one universal gate.
- What is a clipper circuit? Discuss briefly on positive and negative clippers with appropriate sketch and some applications.
- Draw a circuit to explain about R-C phase shift Oscillator.
- State and explain the function of a sweep generator in an oscilloscope.
- How the transistor can be used as an amplifier in CE configuration? Explain with proper diagrams.
- Design a combinational logic circuit which adds three binary bits and implement using NAND gates.
- What are the basic Boolean theorems? State and prove De Morgan's theorem of Boolean algebra.

Part-III

Only Long Answer Type Questions (Answer Any Two out of Four)

210	Q3	Explain how you can use to measure voltage, current, frequency and time period of a sinusoidal wave in CRO. Also write the principle and working of a CRO with a proper block diagram.	(16)	210
210	Q4	Define the terms Input offset voltage, input bias current, CMRR, Slew Rate of an Op-Amp.	(16)	210
	Q5	Define Multiplexing and Demultiplexing. Implement a full adder circuit using two 4:1 multiplexers.	(16)	
	Q6	Draw the circuit of an emitter follower. Derive the expression for input impedance, output impedance and the voltage gain.	(16)	