

Registration No. :

--	--	--	--	--	--	--	--	--	--

Total number of printed pages – 3

B. Tech
PCEL 4301

Fifth Semester Regular Examination – 2014

POWER ELECTRONICS

BRANCH(S) : EEE, ELECTRICAL

QUESTION CODE : H 148

Full Marks – 70

Time : 3 Hours

Answer Question No. 1 which is compulsory and any **five** from the rest.
The figures in the right-hand margin indicate marks.



1. Answer the following questions :

2 × 10

- Enumerate advantages of power BJT over power MOSFET.
- Give protection of SCR against over current.
- What is over drive of power BJT? Why is it not desirable?
- What will be the peak reverse voltage rating of the power switching device used in a 1-phase center tap type full converter if primary supply voltage is 100 V ac (rms) and primary to secondary turn ratio is 1 : 3?
- A single phase fully controlled rectifier has $100 \sin(314t)$ as input supply voltage and resistor R as load. What will be the average output voltage for firing angle of 60° for this rectifier?
- What are the advantages of Cuk converter over Buck-Boost converter?
- At what duty cycle the load ripple current becomes maximum for a Buck converter?
- A 3-phase sine-PWM inverter operates from a dc link voltage of 600 V. What will be the rms magnitude of line voltage of fundamental frequency for modulation index of 1.0.

P.T.O.

- (i) What are the advantages of Space Vector Modulation (SVM)?
- (j) What is trickle charge setting in a battery charger? Why is it necessary?
2. (a) Discuss the turn on and turn off characteristics of IGBT. 5
- (b) What is the totempole configuration of base drive circuit of BJT? In which mode do the transistors in totempole configuration operate? 5
3. (a) Explain with circuit diagram, the BJT triggering scheme. 5
- (b) How is a power BJT protected against 'dv/dt' and 'di/dt'? Explain with relevant circuit diagram. 5
4. (a) A three phase full converter fed from a three phase, 415 V, 50 Hz ac source is connected to load $R = 20 \Omega$, $E = 300 \text{ V}$ and large inductance so that output current is ripple free. Determine the power delivered to load and input power factor for firing angle of 60° . 5
- (b) Derive the expression for average output voltage of three phase fully controlled rectifier feeding R-L load and operating in continuous conduction mode. 5
5. (a) Give a comparison between single phase full converter and single phase semi converter with regards to displacement factor, distortion factor and input power factor presenting relevant waveforms and mathematical expression. 5
- (b) Explain the principle of working of single phase cycloconverter with relevant circuit diagram and waveforms. 5
6. A Boost Regulator has an input voltage of 10V dc. The average output voltage is 30 V and the average output current is 1.0 A. The switching frequency is 25 kHz. If the input side inductance $L=150 \mu\text{H}$ and output side capacitance $C=220 \mu\text{F}$, determine 10
- (a) The duty cycle
- (b) The ripple current of inductor

- (c) The peak current of inductor
- (d) The ripple voltage of filter capacitor.
7. (a) Explain the methods of generating the base/gate drive signals for a single phase sine-PWM voltage source inverter. 5
- (b) With an appropriate power circuit diagram, discuss the working principle of a three phase bridge type voltage source inverter. Draw phase and line voltage wave forms on the assumption that each controlled switch conducts for 120° and three phase resistive load is star connected. 5
8. Write short notes on any two of the following. 5×2
- (a) V-I characteristic of RCT
- (b) AC voltage controller with PWM control
- (c) Buck- Boost regulator
- (d) UPS.
