

Registration No. :

--	--	--	--	--	--	--	--	--	--

Total number of printed pages – 2

B. Tech
CPEC 5303

Fifth Semester (Special) Examination – 2013
ELECTRONICS MEASUREMENT AND MEASURING INSTRUMENTS

BRANCH CODE : EC, ETC

QUESTION CODE : D 311

Full Marks – 70

Time : 3 Hours

*Answer Question No. 1 which is compulsory and any **five** from the rest.
The figures in the right-hand margin indicate marks.*

1. Answer the following questions : 2×10
- (a) Define error.
 - (b) Write the detectors used for DC and AC bridges.
 - (c) Write few advantages of electronics voltmeters.
 - (d) List which can be measured using electronics multimeter.
 - (e) What is meant by signal analysis ?
 - (f) What is a Spectrum ?
 - (g) What is Transducer ?
 - (h) What is meant by data acquisition ?
 - (i) What is meant by interfacing ?
 - (j) What is GPIB Bus ?
2. (a) Define Accuracy, Precision, Resolution, Reliability and Repeatability. 5
- (b) Draw circuit diagram of Maxwell's bridge and derive the expression of unknown components at balanced condition. 5

P.T.O.

3. (a) Draw circuit diagram of amplified DC meter and explain it's operation. 5
 (b) Draw functional block diagram of any one digital voltmeter and explain it's operation. 5
4. (a) Draw functional block diagram of a Wave Analyzer and explain it's operation. 5
 (b) Briefly describe construction and working of a simple frequency counter. 5
5. (a) Briefly describe construction and working of Strain Gauge. 5
 (b) Describe construction and working of any one Displacement Transducer. 5
6. (a) Describe working of a simple Digital Data Acquisition System. 5
 (b) Briefly describe techniques of interfacing transducer to electronics control and measurement system. 5
7. (a) Draw circuit diagram of an Instrumentation Amplifier and derive the expression of it's output voltage. 5
 (b) Draw circuit diagram of an Isolation Amplifier and explain it's operation. 5
8. Write short notes on any two of the following : 5×2
 (a) True rms responding voltmeter-Circuit diagram and operation
 (b) Spectrum Analyzer-Functional block diagram and operation
 (c) Computer Controlled Test system.

