

Registration No. :

--	--	--	--	--	--	--	--	--	--

Total number of printed pages – 2

B. Tech
CPEE 5306

Fifth Semester (Special) Examination – 2013

POWER ELECTRONICS

BRANCH : AEIE, EC, IEE

QUESTION CODE : D 295

Full Marks – 70

Time : 3 Hours

Answer Question No. 1 which is compulsory and any **five** from the rest.

The figures in the right-hand margin indicate marks.

1. Answer the following questions : 2 × 10
- Draw the V-I characteristic of an IGBT.
 - What is the advantage of cosine law triggering scheme ?
 - Explain the function of snubber circuit.
 - What is non repetitive peak reverse voltage rating of SCR ?
 - How is the reactive power of a 1-Ph fully controlled rectifier affected by the firing angle?
 - Draw the source current wave form for a single phase semi converter feeding R-L load under the assumption that the load current is continuous and ripple free having a value of 20 A and for a firing angle of 60° . Find the rms value of thyristor current.
 - Give the advantages of Voltage Source Inverter over Current Source Inverter.
 - Give the chopper circuit for regenerative braking of DC motor.
 - What are the advantages of 180° conduction mode 3-Phase VSI over 120° conduction mode ?
 - Give two advantages of HVDC transmission.
2. (a) Draw the gate characteristic of SCR and explain its gate protection circuit. 5
- (b) What are the various problems that arise in the series operation of SCRs ? How are they overcome ? 5

P.T.O.

3. (a) Explain with relevant circuit diagram and waveforms the operation of UJT triggering scheme. 5
- (b) Explain the load commutation principle for a thyristor based system with suitable circuit diagram and relevant waveforms. 5
4. (a) What are the merits and demerits of semi converter over full converter? 5
- (b) A single phase full converter feeding RL load has the following data. Source voltage = 230 V 50 Hz, $R=10\ \Omega$, firing angle = 45° . If the load inductance is large enough to make the load current virtually constant, compute : 5
- (i) the average value of load voltage and load current.
- (ii) the input power factor
5. For a 3-Phase fully controlled bridge rectifier operating from a 3-Phase, 415 V, 50 Hz supply with inductive load, derive the following : 10
- (a) average output voltage
- (b) rms output voltage
- (c) distortion factor
- (d) harmonic factor
- (e) transformer utilization factor(TUF)
6. (a) Explain the working of a parallel inverter employing feedback diodes with the help of neat circuit diagram and relevant waveforms. 5
- (b) Compare between voltage source inverter and current source inverter. 5
7. (a) Explain the operation of a auxiliary voltage commutated chopper with circuit diagram and relevant waveforms. 5
- (b) Explain the operational principle of integral cycle triggering. 5
8. Write short notes on any **two** of the following : 5x2
- (a) Static V-I characteristics of GTO
- (b) Effect of source inductance in the performance of full converter
- (c) Modified Mc-Murray Bedford inverter
- (d) UPS.

