

Registration No. :

--	--	--	--	--	--	--	--	--	--

Total number of printed pages – 2

B. Tech
CPEC 5306

Sixth Semester (Special) Examination – 2013

ADVANCED ELECTRONICS CIRCUITS

BRANCH : EC

QUESTION CODE : E 304

Full Marks – 70

Time : 3 Hours

Answer Question No. 1 which is compulsory and any **five** from the rest.

The figures in the right-hand margin indicate marks.

1. Answer the following questions : 2 × 10
- How quality factors (Q) is related with bandwidth of band pass filter ?
 - What is the cut off frequency of an op-amp if the unity-gain bandwidth is 1 MHz and the open-loop voltage gain is 10^5 ?
 - What is a multivibrator ? What is its physical significance in electronics circuits?
 - Write the transfer function of the 2nd order filter ? Find 3-dB frequency from the transfer function.
 - What is the basic principle of a phase detector (PD) of a PLL?
 - Define sweep speed error. Give an expression.
 - Define capture range of a phase locked loop (PLL)? What is its importance?
 - What is triggering in multivibrator ? Mention different methods of triggering used in multivibrator ?
 - Draw the characteristic waveform of UJT.
 - What is roll off rate (ROR) of an active filter ? How it effects the performance of a filter ?
2. (a) What is a phase detector (PD) ? With neat diagram, explain the principle operation of a PD. 5

P.T.O.

- (b) Explain the principle operation of a 2nd order phase locked loop (PLL) . Derive its transfer function. 5
3. (a) What is a time base voltage ? With a neat diagram, explain the principle of a transistor current time base generator ? 5
- (b) Explain the basic principle of an oscillator ? What are the conditions to be fulfilled to obtain steady oscillation at a fixed frequency ? 5
4. (a) Explain with a neat sketch the operation principle of a monostable multivibrator with waveforms. 5
- (b) Design low pass filter at a cut-off frequency of 20 KHz with a pass band gain of 10. Justify the component values you use. 5
5. (a) What is a Notch filter ? What is its importance ? Explain in detail a notch filter and then find its transfer function. 5
- (b) Design a all-pass filter, and determine the phase shift between the input and output at $f = 2$ KHz. To obtain a positive phase shift, what modifications are necessary in the circuit ? 5
6. (a) What is a voltage comparator circuit ? What are the characteristics of a voltage comparator ? Explain how OPAMP can be used as a voltage comparator. 5
- (b) With a neat diagram, explain wein-bridge oscillator ? 5
7. (a) What is a Schmitt trigger circuits ? Discuss various applications of Schmitt trigger circuits. 5
- (b) What do you mean by triggering of multivibrators ? What are the various methods to trigger the bistable multivibrators ? 5
8. Write short notes on any **two** : 5 × 2
- (a) Voltage controlled oscillator (VCO)
- (b) Active and passive filters
- (c) IC 555
- (d) All pass filter.

