

Registration No. :

Total number of printed pages – 4

B. Tech
BEES 2211

Special Examination – 2012

NETWORK THEORY

Full Marks – 70


Time : 3 Hours

Answer Question No. 1 which is compulsory and any **five** from the rest.

The figures in the right-hand margin indicate marks.

1. Answer the following questions : 2 × 10

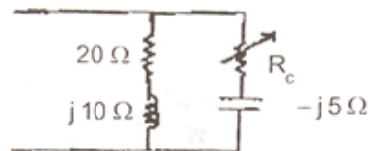- (a) What do you understand by a 'oriented graph' ?
- (b) Calculate the value of R_c in the circuit shown below to yield resonance.



- (c) Two coils in differential connection have self inductance of 2 mH and 4 mH and a mutual inductance of 0.2 mH. What will be the equivalent inductance ?
- (d) Distinguish between Fourier transform and Laplace transform.
- (e) Mention the properties of RL driving point impedance.
- (f) Laplace transform of a function $F(t)$ is given as $\frac{s^2 + 2s + 3}{(s^3 + 3s^2 + 3s + 1)}$. Find $F(0)$ and $F(\infty)$.
- (g) What is Foster reactance theorem ?

P.T.O.

- (h) For a π network having series impedances as Z_1 and shunt impedance is $2Z_2$. What is the image impedance ?
- (i) Z parameter of a 2 port network are $Z_{11} = 10 \Omega$, $Z_{22} = 20 \Omega$, $Z_{12} = Z_{21} = 5 \Omega$. Find the A, B, C, D parameters.
- (j) Why Y parameters are known as short circuit parameters ?
2. (a) State and explain Milliman's Theorem. 5
- (b) For the network shown in figure 2(b). Calculate the maximum power that may be dissipated in the external resistor R. 5

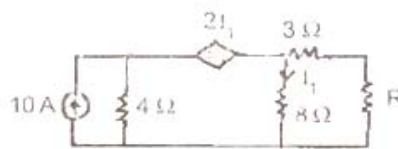


Fig. 2(b)

3. (a) For the network shown in fig. 3(a) below, determine the No. of branches, number of nodes and number of links. Also write down the incidence matrix for the network. 5

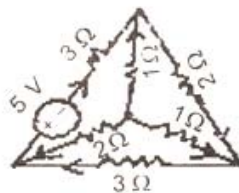


Fig. 3 (a)

- (b) Determine the the values R, L and C in a series RLC circuit that resonates at 2 kHz and consumes 100 W from a 100 V AC source operating at the resonance frequency. The bandwidth is 0.75 kHz. Find the half power frequencies. 5
4. (a) In the network shown fig. 4(a) the capacitor C has an initial voltage $V_c = 10 \text{ V}$ and at the same instant, the current through the inductor L is zero,

the switch S is closed at time $t = 0$. Find out the expression for the voltage $v(t)$ across the inductor. 5

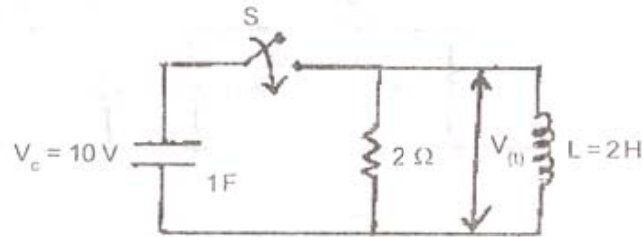


Fig. 4(a)

(b) In the two mesh network shown in Fig. 4(b) below, there is no initial charge on the capacitor. Find the loop currents $i_1(t)$ and $i_2(t)$ which results when the switch is closed at $t = 0$? (use Laplace transform) 5

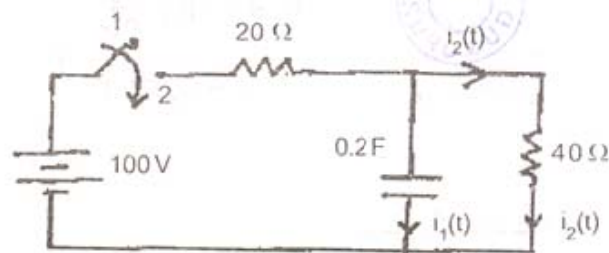


Fig. 4(b)

5. (a) Determine the Fourier transform of this $v(t)$ shown in Fig. 5(a) and also sketch the continuous amplitude and phase spectra of this $v(t)$. 5

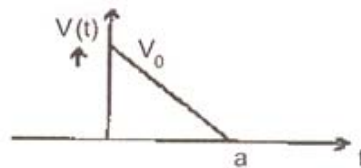


Fig. 5(a)

(b) Find the inverse Laplace transform of the function given below : 5

$$\frac{12}{(s+2)^2(s+4)}$$

6. (a) Calculate the Y parameters for the network shown in Fig. 6(a). 5

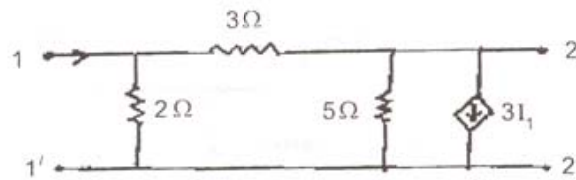


Fig. 6 (a)

- (b) Examine whether the network function $F(s) = \frac{3s^3 + s^2 + 2s + 4}{(s+2)(s+4)}$ is positive real. 5
7. (a) Realize the function $Y(s) = \frac{s(s+3)}{6(s+2)(s+4)}$ Cauerl form. 5
- (b) Realize the network function given by $F(s) = \frac{(s+1)(s+3)}{s(s+2)}$ in the Foster-I form. 5
8. Write short notes on any **two** : 5×2
- Tellegen's theorem
 - Restriction on location of Poles and Zeros
 - Positive Real Function and explain its properties.