

Registration No. :

--	--	--	--	--	--	--	--	--	--

Total number of printed pages – 4

B. Tech  
CPES 5201

## Special Examination – 2012

### NETWORK THEORY

Full Marks – 70

Time : 3 Hours

Answer Question No. 1 which is compulsory and any **five** from the rest.

The figures in the right-hand margin indicate marks.

1. Answer the following questions : 2 × 10

- (a) Write down two properties cut set ?
- (b) State Maximum power transfer Theorem ?
- (c) What do you mean by mutual inductance ? Explain.
- (d) Write down the relation between links and twigs.
- (e) Why a step signal is preferred input for study of transient response ?
- (f) Discuss two utilities of fourier series in network theory.
- (g) The transmission parameter equation of a two port device is defined by the following pair of equations :

$$V_1 = 5V_2 - 2I_2, I_1 = 4V_2 - 3I_2.$$

Write its impedances parameter  $Z_{11}, Z_{12}, Z_{21}, Z_{22}$ .

- (h) Draw the circuit for a second order active low pass filter.
- (i) Write down two applications of active filter ?

(j) Check whether  $F(s) = \frac{2S^2 + S + 1}{S^2 + 2S + 1}$  is a positive real function.

P.T.O.

2. (a) What do you understand by dot convention for representing the mutually coupled coils ? Explain in brief by drawing a circuit showing dot convention. 5

- (b) For the network shown in Fig 2 (b), draw the oriented graph and obtain the tie set matrix. Also use this matrix to calculate the current  $i$ . 5

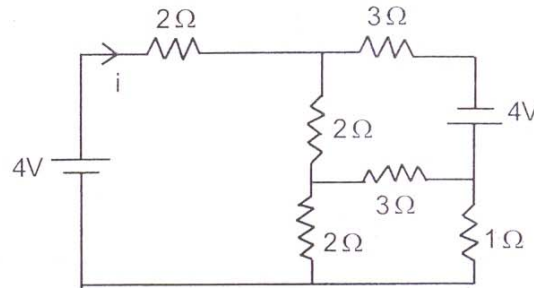


Fig 2(b)

3. (a) Verify the Reciprocity Theorem for the network shown below in Fig 3(a). Using current source as shown and  $v_1$  is the voltmeter reading. 5

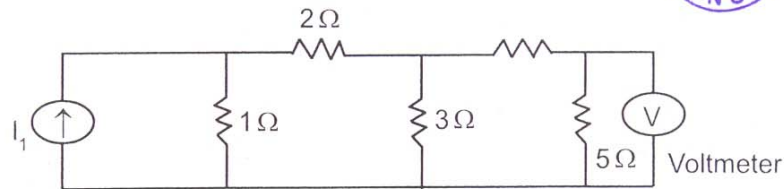


Fig 3(a)

- (b) A current source, having an internal resistance of  $5k\Omega$  feeds a tank circuit containing a coil having  $L = 200\text{ mH}$  and  $R = 20\Omega$  in parallel to a capacitor of  $200\mu\text{ F}$ . Find the frequency of resonance and Q factor. 5
4. (a) Determine the complex frequency  $S$  of each term : 5
- (i)  $v(t) = 8 + 2\cos t\text{ mV}$
  - (ii)  $v(t) = 65e^{-1000t}\cos 1000t\text{ V}$
  - (iii)  $q(t) = 7e^{-5t}\text{ C}$
  - (iv)  $q(t) = 7e^{-5t} - 19e^{-5t}\sin(8t - 42^\circ)\text{ C}$

- (b) In the network shown Fig 4(b) the switch is closed and a steady state is reached in the network. At time  $t = 0$  the switch is opened. Find the expression for the current through the inductor  $i_2(t)$  ? 5

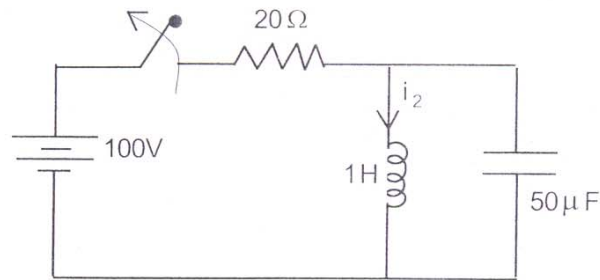


Fig 4(b)

5. (a) Determine the fourier series expansion of the function for the wave form shown below in Fig 5(a). 5

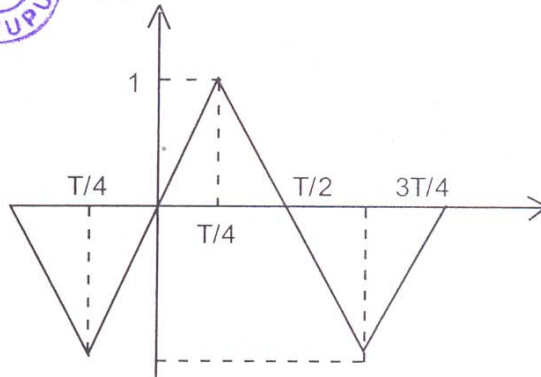


Fig 5(a)

- (b) Obtain the fourier coefficients for the function given by  $f(t) = (t + \pi)$  when  $-\pi < t < \pi$  ;  $f(x + 2\pi) = f(x)$ . 5
6. (a) Determine the Z parameter for the bridged T network shown in Fig 6 (a) below. 5

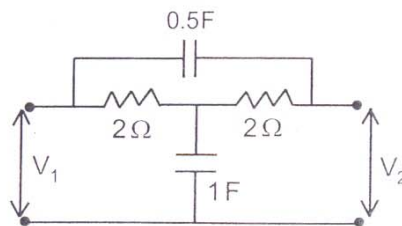


Fig 6(a)

- (b) What are the limitations on pole and zero locations in transfer function? 5
7. (a) Design a constant k high pass filter having a cut off frequency of 1500 Hz. The resistance of the load circuit is  $600\Omega$ . Determine the values of components required? 5
- (b) Synthesize the impedance function  $Z(s) = \frac{s(s^2 + 3)(s^2 + 5)}{(s^2 + 2)(s^2 + 4)}$  Using Cauer II form? 5
8. Write short notes on any **two**: 5×2
- (a) Band width and Selectivity
  - (b) Milliman's Theorem
  - (c) Final value theorem