

Registration No :

--	--	--	--	--	--	--	--	--	--

Total Number of Pages:02

B.TECH
PEE31102

3rd Semester Back Examination: 2019-20
ANALOG ELECTRONICS CIRCUIT
BRANCH : ELECTRICAL

Marks : 100

Time : 3 Hours

Q.Code : HB528

Answer Question No.1 (Part-1) which is compulsory, any eight from Part-II and any two from Part-III.

The figures in the right hand margin indicate marks.

Part- I

Q1 Only Short Answer Type Questions (Answer All-10) (02x10)

Suggested Words: How, Why, Determine, Derive, State, Write, Create, etc

- With the help of mathematical equation show how the load line is varying with R_c .
- With the help of neat sketch show the prohibited regions of Q-point?
- What is the need for biasing?
- Define the pinch off voltage in JFET.
- Derive the relationship of g_m and g_{m0} using Shockley's equation.
- Two BJTs with $\beta_1=80$ & $\beta_2=120$ form a Darlington pair. What is the overall β of the Darlington pair?
- Write the major two differences between BJT and JFET.
- Write the significance of the current Mirror in practical application?
- State the two application of emitter follower circuit.
- Which configuration is used as a current Buffer? Justify.

Part- II

Q2 Only Focused-Short Answer Type Questions- (Answer Any Eight out of Twelve) (06x08)

Analyze, Justify, Design, Formulate, Calculate, Develop, Illustrate, Explain, Distinguish, Differences & Similarities

In square wave testing of an audio amplifier a 5kHz square wave signal was applied at the input of the amplifier. The output wave form seen on the screen of


- oscilloscope records 10% rise of amplitude in 20microsec and 90% rise in 80microsec. Determine the bandwidth of the amplifier?
- Explain with the help of neat sketches how h-parameters can be determined graphically from the i/p & o/p characteristics of BJT

For the JFET network given that $g_m= 2.2mS$.

Sketch the two port model by calculating

AV_{NL} , Z_i , Z_o , and calculate A_v and A_{vs}

c)

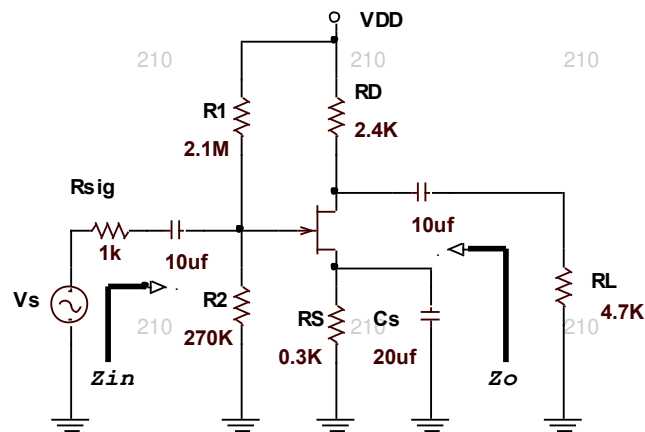

- Explain various advantages of negative feedback? Draw the block diagrams of different feedback topologies?

- e) What is the concept of virtual ground? Using this concept derive the expressions for the closed loop gain of inverting and non inverting amplifier using op-amp.
- f) Derive the condition of oscillation and expression for the output frequency for a Wien bridge oscillator using op-amp.
- g) Formulate the relationship of upper cut off frequency with that of the rise time of an amplifier.
- h) Analyse the impact of physical capacitor on the low frequency response of an amplifier.
- i) Differentiate between casecade and cascode amplifier with neat circuit diagram.
- j) Illustrate the operation and construction of a CMOS inverter?
- k) Differentiate the power amplifier ? Why it is called large signal amplifier?
The input power to a device is 10000W at a voltage of 1000V. The output power is 500W, while the output impedance is 20Ω . Find the power gain and voltage gain in decibel.

Part-III

Only Long Answer Type Questions (Answer Any Two out of Four) (02X16)

Discuss, Describe, Examine, Classify, Prove, Evaluate, Compare, Contrast, etc

- What is instrumentation amplifier? What are the properties of a good instrumentation amplifier?
- Q3** Derive the output voltage equation of a standard instrumentation amplifier?
- Q4** Describe the construction, operation and V-I characteristics of a n-channel JFET?
- Q5** What are the characteristics of an ideal opamp. Discuss various important parameters.
- Q6** Compare the CE amplifier with bypassed and unbypassed emitter capacitor. Analyse with the help of circuit diagram and mathematical expressions of their voltage gain and input impedance,