



Registration No:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 2

AR-17

B.TECH

3rd Semester (BACK PAPER) Examination-2019**BECES3050 DIGITAL LOGIC DESIGN**

Common to CSE/IT

Time : 3 Hours

Maximum : 100 Marks

Answer ALL Questions

The figures in the right hand margin indicate marks.

PART – A: (Multiple Choice Questions) 10 x 2=20 Mark**Q.1. Answer All Questions**

- a How many input combinations would a truth table has for a six-input AND gate?
a) 32 b)48 c) 64 d) 80
- b The expression $W(X + YZ)$ can be converted to SOP form by applying which law?
a) associative law b) commutative law c) distributive law d) none of the above
- c The 2's complement of 11100111 is _____.
a) 11100110 b) 00011001 c) 00011000 d) 00011010
- d What logic function is the sum output of a half-adder?
a) OR b) NOR c) exclusive-OR d) exclusive-NOR
- e A full-adder has a $C_{in} = 0$. What are the sum (Σ) and the carry (C_{out}) when $A = 1$ and $B = 1$?
a) $\Sigma = 0, C_{out} = 0$ b) $\Sigma = 0, C_{out} = 1$ c) $\Sigma = 1, C_{out} = 0$ d) $\Sigma = 1, C_{out} = 1$
- f Which gate is best used as a basic comparator?
a) OR b) NOR c) Exclusive-OR d) Exclusive-NOR
- g A BCD counter is a _____.
a) binary counter b) full-modulus counter c) decade counter d) divide-by-100 counter
- h How many flip-flops are required to construct a decade counter?
a) 10 b) 8 c) 6 d) 4
- i Dynamic memory cells store a data bit in a _____.
a) Capacitor b) Diode c) Flip-Flop d) Resistor
- j How many $8K \times 1$ RAMs are required to achieve a memory with a word capacity of 8K and a word length of eight bits?
a) Eight b) Four c) Two d) One

PART – B: (Short Answer Questions) 10X2=20 Marks**Q.2. Answer All questions**

- a What is gray code? Convert $(100110101)_2$ into gray code.
- b What is the decimal equivalent of the binary number $(1000\ 1011\ 0111)$ represented in Excess-3 code?
- c State De Morgan's law?
- d Consider the function $f(x_1, x_2, x_3) = \Sigma m(2, 3, 4, 6, 7)$. Derive the canonical sum-of-product for the function using minterm.
- e What do you mean by "Prime Implicants" in a Karnaugh map? Under what condition a min-term in a square is said to be essential?
- f Implement the following Boolean expression with X-OR and AND gates.
 $F = AB'CD' + A'BCD' + AB'C'D + A'BC'D$
- g How many clock pulses are required shift eight bits of data into and out of an eight bit serial-in serial-out shift register?
- h What is a shift register? Explain the principle of 4-bit parallel-in parallel-out shift register.
- i List the various types of DACs and ADCs.
- j Which is the simplest type ADC? What is its other name?

PART – C: (Long Answer Questions) 4X15=60 Marks



Answer ALL questions

- Q.3**
- a Convert the decimal number 4.532×10^7 to a single-precision floating-point binary number. 7
 - b Establish the following identities of Boolean algebra 8
 - (i) $A + AB = A$
 - (ii) $(A + B)(A + C) = A + BC$
- OR
- c In a tabular form, write the “2421” code and “Excess-3” code of decimal digit “0 to 9”. What are the special properties of these codes? 7
 - d Simplify the following Boolean expression using Boolean algebra: 8
 - (i) $x'y'z + x'yz + xy'$
 - (ii) $xyz + x'z + yz$
- Q.4**
- a The four variable logic function can be expressed as 10

$$F(A, B, C, D) = \Sigma m(1, 2, 5, 7, 9, 11, 14).$$
 Realize the above function using
 - (i) NAND gates only
 - (ii) NOR gates only.
 - b Implement the following Boolean function using NAND-AND two level combinational form 5

$$F(A, B, C, D) = \Sigma m(0, 1, 2, 3, 4, 8, 9, 12)$$
- OR
- c Implement the following Boolean function using 4 x 1 MUX : 7

$$F = A'B'C + ABC + ABC + ABC$$
 - d The four variable logic function can be expressed as 8

$$F(A, B, C, D) = \Sigma m(1, 2, 5, 7, 9, 11, 14).$$
 Realize the above function using 8 x 1 MUX.
- Q.5**
- a What is a shift register? Explain the principle of a 4-bit Serial-in Parallel-out shift register. 5
 - b An 8-bit shift register has the binary equivalent of the decimal number 86 stored in it. What are the base-10 equivalent contents of the register after the following operations have been performed? For each case, assume the same initial state given. 10
 - (i) Shift Right 1 (ii) Shift Left 1 (iii) Shift Right 2 (iv) Rotate Right 2 (v) Rotate Left 2
- OR
- c A sequential circuit with two D Flip-flops A and B. two inputs in: and y and one output z is specified by the following state equations. 10

$$A(t+1) = x'y + xA \quad B(t+1) = x'B + xA \quad Z = B$$
 - (i) Draw the-logic diagram of the sequential circuit.
 - (ii) Derive state table.
 - (iii) Draw the state diagram.
 - (iv) Derive the flip-flop input functions.
 - d Design a sequential circuit with two D flip-flops A and B and one input X. When X = 0, the state of the circuit remains same. When X = 1, the circuit goes through the state transition from 00 to 01 to 11 to 10 d back to 00 and repeats. 5
- Q.6**
- a What is Hamming code? Explain, how error is detected and corrected at the receiving end using hamming code? 7
 - b Explain briefly basic configuration of programmable logic devices (PLD). 8
- OR
- c How many 32K x 8 RAM chips are needed to provide a memory capacity of 256 K bytes? How many lines of the address must be used to access 256K bytes? How many of these lines are connected to the address inputs of all chips? 7
 - d Draw the diagram of the 4 x 4 RAM. 8