



Registration No:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 2

AR-17

B.TECH

3rd Semester (BACK PAPER) Examination-2019**BEEPC3020 NETWORK THEORY**

EE/EEE

Time : 3 Hours

Maximum : 100 Marks

Answer ALL Questions

The figures in the right hand margin indicate marks.

PART – A: (Multiple Choice Questions) 10 x 2=20 MarkQ.1. Answer All Questions

- a In Superposition theorem, while considering a source, all other voltage sources are?
a) open circuit b) short circuited c) change its position d) removed from the circuit
- b Superposition theorem states that the response in any element is the _____ of the responses that can be expected to flow if each source acts independently of other sources.
a) algebraic sum b) vector sum c) multiplication d) subtraction
- c If z-parameters are $z_{11} = 40$, $z_{22} = 50$ and $z_{12} = z_{21} = 20$, what would be the value of y_{22}
a. 4 / 160 b. 5 / 160 c. 10 / 160 d. 15 / 150
- d Which is the correct condition of symmetry observed in z-parameters?
a. $z_{11} = z_{22}$ b. $z_{11} = z_{12}$ c. $z_{12} = z_{22}$ d. $z_{12} = z_{21}$
- e An open circuit reverse voltage gain in h-parameters is a unit less quantity and generally equivalent to _____
a. V_1 / I_1 (keeping $V_2 = 0$) b. I_2 / I_1 (keeping $V_2 = 0$)
c. V_1 / V_2 (keeping $I_1 = 0$) d. I_2 / V_2 (keeping $I_1 = 0$)
- f In a certain parallel resonant band-pass filter, the resonant frequency is 14 kHz. If the bandwidth is 4 kHz, the lower frequency is
a) 7 kHz b) 10 kHz c) 12 kHz d) cannot be determined
- g In a series resonant band-pass filter, a lower value of Q results in
a) a higher resonant frequency b) a smaller bandwidth
c) a higher impedance d) a larger bandwidth
- h If there are 5 branches and 4 nodes in graph, then the number of mesh equations that can be formed are?
a) 2 b) 4 c) 6 d) 8
- i The dual pair of capacitance is?
a) capacitance b) resistance
c) current source d) inductance
- j How many fundamental cutsets will be generated for a graph with 'n' number of nodes?
a. n+1 b. n-1 c. $n^2(n-1)$ d. n/ n-1

PART – B: (Short Answer Questions) 10X2=20 MarksQ.2. Answer All questions

- a Which theorem obeys laws of conservation of energy?
- b Under what condition Norton theorem is applicable.
- c State and explain Thevenin's theorem.
- d Distinguish between steady state and transient response.
- e What is the significance of time constant of R-L circuit?
- f A system has input unit step and transfer function
$$\mathcal{T}(s) = \frac{1}{s^2 + 3s + 5}$$
 Find output of the system at steady state
- g What are critical frequencies ? Why they are so called ?
- h In a given RL type high pass filter $R = 3 \text{ K}\Omega$ and $f_c = 2000 \text{ KHz}$. Find out the value of L.
- i Mention the properties of RC driving point impedance.
- j List three properties of positive real function

**PART – C: (Long Answer Questions) 4X15=60 Marks****Answer ALL questions**

- Q.3**
 a Write short note any Compensation theorem. 7
 b Write short note any Tellegen's theorem. 8

OR

- c State & explain Superposition Theorem. 7
 d Define Thevenin's theorem with example. 8

- Q.4**
 a A network function is given as

$$I(s) = \frac{2s}{(s+1)(s+2)}$$
 7

Obtain the time-domain response from the pole-zero plot.

- b Describe the Time domain behavior from Pole-Zero 8

OR


- c What information do poles and zeros provide in respect of network to which they relate? 7
 d Explain different restriction on location of poles and zeros for a driving point function. 8

- Q.5**
 a Design a low pass filter as π - and T-networks having a cutoff frequency $f_c = 1000\text{Hz}$ to operate with a terminated load resistance of 200Ω . Also find the frequency at which this filter offers attenuation of 19.1 dB. 7
 b Design a constant K-type HPF filter (both T & π) having nominal impedance of 700Ω and cut-off frequency of 6000Hz . Also determine the characteristic impedance, attenuation constant and Phase shift at 4000Hz & 10000Hz . 8

OR

- c Design a constant K band pass filter with cutoff frequencies 3kHz and 7.5kHz and nominal characteristic impedance of 900Ω . 7
 d Design a constant K band stop filter with cutoff frequencies 3kHz and 7.5kHz and nominal characteristic impedance of 900Ω . 8

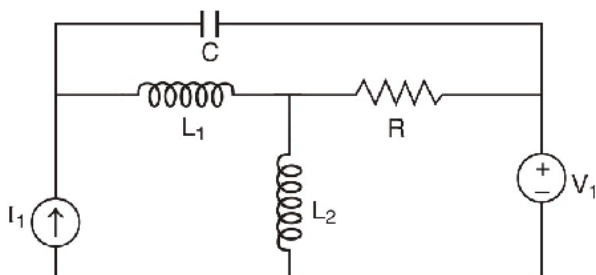- Q.6**
 a For the network shown in fig., determine incidence matrix. Also find number of trees possible for the network.



- b Write short answer on Cut set and Tie Set Matrix. 8

OR

- c Check whether the polynomial is Positive Real 7

$$F(s) = \frac{2s^2 + 2s + 1}{s^3 + 2s^2 + s + 2}$$

- d Using Foster Form II, synthesis the function. 8

$$Y(s) = \frac{(s^2 + 5)(s^2 + 13)}{s(s^2 + 9)} \\ ==0==$$

