



Roll No:

--	--	--	--	--	--

AR-18

Total Number of Pages : 2

M. Sc

M. Sc 3rd SEMESTER REGULAR EXAMINATIONS, NOV/DEC 2019-20

Subject code: CEC-PHY-302

Subject: Electronics

Time: 3 Hours

Max Marks: 80

The figures in the right hand margin indicate marks.

SECTION A

Q.1 Answer any four of the following:

[4 X4 =16]

- a What is the expression for voltage gain in common source npn JFET amplifier?
- b Write brief notes on MOSFET.
- c Explain the following things of an operational amplifier.
 - a. Input bias current
 - b. Input offset current
 - c. Base current
 - d. Input offset voltage
- d What do you mean by CMMR?
- e Find out the expression for the output voltage of a summing circuit having inputs given to both inverting and non inverting ends. Assume two resistors are connected on each input.
- f What is the logic circuit whose Boolean equation is $Y = \bar{A}BC + A\bar{B}C$?

Or

2. Answer all questions from the following

[8×2 =16]

- a If the DC emitter current of a npn transistor is 0.83 mA, then what is the value of ac resistance of the emitter diode?
- b What are the advantages of hybrid parameter?
- c In a phase shift oscillator the value of $R = R_L$ is $4.7k\Omega$ and capacitance $C = 0.01\mu F$. Determine the frequency of oscillator.
- d How to use an operational amplifier as a unit gain buffer circuit?
- e Construct an integrator and a differentiator circuit using operational amplifier.
- f Construct an XOR gate and write the truth table for the same.
- g What are the output voltages caused by each bit in a 5-bit ladder if the input levels are $0 = 0 V$ and $1 = + 10 V$?
- h Find the binary equivalent weight of each bit in a 4-bit system.



SECTION-B

3. Answer all Questions: [4 × 16 = 64]
- a Draw the drain characteristic curve and transconductance curve for a neatly drawn npn JFET and explain the different regions of the drain characteristic curve. 16
- OR
- b What are the four different types of biasing methods followed in the active region of a npn JFET? Explain each of them in detail. 16
- 4.
- a Find out the voltage gain expression of a differential amplifier by using non inverting input and single-ended output using a neat circuit diagram. What is the expression of input impedance in the same circuit? 16
- OR
- b Find out the expression of gain, input impedance, bandwidth for an inverting and a non inverting negative feedback operational amplifier without using any approximation. 16
- 5.
- a Draw the circuit diagram of Wien bridge oscillator with a neat circuit diagram and explain how it generates a large range of frequencies. 16
- OR
- b How to construct a quartz crystal oscillator? Explain various important physical properties of the crystal to achieve a better oscillator. Draw an equivalent circuit of a vibrating crystal and find out the resonant frequency of the circuit. 16
- 6.
- a Construct NOT, OR, AND gates by using the universal gates. Write the corresponding truth table for them. Explain De Morgan's theorem. 16
- OR
- b Explain the principle of conversion of analog signal to digital signal by using binary ladder method. 16