



Registration No:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 02

M.TECH

AR-17

M.TECH 1<sup>ST</sup> SEMESTER EXAMINATIONS(BACK), NOV/DEC 2019

PE, MPEPC1030

POWER CONVERSION DEVICES AND DRIVES

Time: 3 Hours

Max Marks : 70

The figures in the right hand margin indicate marks.

**PART-A****(10 X 2=20 MARKS)****1. Answer the following questions.**

- What are the voltage equations in the rotor's dq0 reference frame for Synchronous motor
- Draw the steady state characteristics of Induction machines
- Draw the basic Two-pole Machine representation of Commutator machines
- Draw the approximate transient torque characteristics of Synchronous machine
- Write the voltage and current equations of Kron's Primitive machine
- What are the advantages of single phase bridge converter over single phase mid-point converter?
- Give an expression for average voltage of single phase semi converters.
- What is meant by natural commutation?
- What types of inverters require feedback diodes?
- What are the control strategies for chopper?

**PART-B****(5 X 10=50 MARKS)****Answer any five questions from the following.**

- Q2. a. Explain the Leakage fluxes in a machine with more than two windings.
- b. Explain how a differential equation for an A.C. circuit or machine can be converted to a phasor equation
- Q3. a. Explain induction motor dynamics during starting and braking.
- b. Explain the two-axis representation of a synchronous machine
- Q4. a. Briefly explain the vector control of induction motors
- b. Draw the equivalent circuit for a single phase induction motor based on the two revolving field theory and identify the various parameters involved in it.
- Q5. a. What is an inverter? What help of circuit and waveforms explain the operation of single Phase bridge inverter.
- b. Draw the waveforms and discuss the performance of Sinusoidal PWM control used in



inverters.

- Q6. a. Explain the operation of three phase fully controlled rectifier with R Load for a firing angle of  $90^\circ$ . Sketch the waveforms of
- Output voltage
  - Load current
  - Voltage across thyristors
- b. Define Chopper. What are the different types of Choppers? Explain its four quadrant operation
- Q7. a. With neat diagram describe the static Scherbius method for slip recovery power for three-phase induction motor. What are its advantages over Kramer's drive
- b. Derive the Torque speed characteristics of 3-phase induction motor drive
- Q8. a. Draw and explain the labelled block diagram of PWM control method of induction motor. Write any two advantages of it.
- b. What are the Components of power electronic Drives. Explain the Criteria for selection of Drive components

**==0==**