



Registration No:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 1

M.TECH

M.TECH 3rd SEMESTER REGULAR EXAMINATIONS, NOV / DEC 2019

MPEPE3012 – FACTS AND CUSTOM POWER DEVICES

(Power Electronics)

Time: 3 Hours

Max Marks : 70

PART-A

(10 X 2=20 MARKS)

1. Answer the following questions.

- Define Sub synchronous resonance
- What is the need of using power electronics based regulators.
- Give the block diagram for a basic IPFC control scheme
- Draw the VI characteristics of SVC.
- What is PWM converter & what are its advantages
- What are the objectives of shunt compensation
- What are the different methods to control flow of power in a parallel path in electrical power systems
- What are the advantages of GCSC?
- What is IPFC?
- What are static VAR generators?

PART-B

(5 X 10=50 MARKS)

Answer any five questions from the following.

- With a neat circuit diagram and waveforms, explain the operation of full wave bridge converter. 5
- Discuss details about different Configuration of SVC. 5
- Write Short notes on static VAR generators. 5
 - With phasor diagram and power-angle curves, discuss midpoint voltage regulation of a transmission line. 5
- Describe the effect of series and shunt compensation at mid-point of the line. 5
 - List different series FACTS converters. With neat circuit diagrams, discuss the operation of Thyristor switched series capacitor (TSSC), and thyristor controlled series capacitor (TCSC). 5
- Define UPFC. Derive the modeling of UPFC for power flow studies. 5
 - Explain the transient stability enhancement and power oscillation damping of SMIB system with SVC connected at the mid-point of the line. 5
- Explain the basic concept of voltage regulator with the help of a phasor diagram. 5
 - Explain the operation of variable impedance type static var generators. 5
- What are the advantages of three-phase converters over single-phase converters? 5
 - Analyse the modeling of TCSC to enhance the stability of the system. 5
- What is the importance of pulse number of a converter? Discuss the transformer connections for 12 pulse and 24 pulse operation of a converter. 5
 - Explain the basic concept of phase angle regulator with the help of a phasor diagram. 5