

--	--	--	--	--	--	--	--	--	--

Registration no:

Total Number of Pages: 02

B.TECH

PCEC4401

7th Semester Regular / Back Examination 2015-16

VLSI DESIGN

BRANCH: AEIE,EC,ETC,IEE

Time: 3 Hours


Max marks: 70

Q.CODE: T188

Answer Question No.1 which is compulsory and any five from the rest.

The figures in the right hand margin indicate marks.

 - Q1 Answer the following questions: (2 x 10)**
- a) Show the basic structure of a MOS transistor.
 - b) What are the three regions of operation of a MOS transistor?
 - c) What is Body effect?
 - d) What is the use of the LOCOS technology? Mention its pros and cons.?
 - e) Define propagation Delay time with suitable illustration.
 - f) What is the importance of monolithic integration?
 - g) What are the drawbacks of resistive load inverter? How can they be overcome?
 - h) Sketch a transistor level schematic of a CMOS 3-input XOR gate. Assume that both the true and complementary versions of the inputs are available.
 - i) Write down at least two advantages and two disadvantages of the pseudo-*n*MOS logic compared to the CMOS logic.
 - j) Give the schematic of XILINX Configurable Logic Block (CLB).
- Q2 a) Compare the constant field and constant voltage scaling approaches in terms of area, delay, energy and power density parameters. (5)**
- b) Draw a neat sketch of the *Y-chart* (or the Gajski Chart) to illustrate the VLSI design domains. (5)**
- Q3 a) What are DC voltage transfer characteristics and noise margins? How do noise margins change with increase in the p-transistor width relative to that of n-transistor? (5)**
- b) Write briefly the limitations of scaling in MOS VLSI design. (5)**
- Q4 Consider the CMOS inverter circuit in Figure Q4 with the following parameters. Assume long channel transistors and no velocity saturation. Given- $V_{DD}=3.3$ V, $k_n=200\mu A/V^2$, $k_p=80\mu A/V^2$, $V_{T0n}=0.6$ V, $V_{T0p}=0.7$ V. (10)**



Find V_{OL} , V_{OH} , V_{IL} , and V_{IH} on the VTC. Also find the noise margins of this inverter.

- Q5 a)** Implement the equation $X = ((A'+B') (C'+ D'+E') +F')G'$ using complementary CMOS using minimum number of transistors. **(5)**
- b)** A polysilicon trace that is $0.6\mu\text{m}$ wide, 0.05mm long, and $0.5\mu\text{m}$ thick has a sheet resistance of 20Ω . It is used to form a high frequency signal trace. **(5)**
- i) What is sheet resistance? Calculate the resistance of the poly trace.
- ii) Calculate the line capacitance of this signal trace assuming the line is separated from a conducting plate by a 100\AA thick oxide layer. Express your answer in fF (10-15)
- iii) Calculate the time constant (RC-delay) associated with this trace. What does this result indicate?
- Q6 a)** If a domino gate input is initially a '1' at the start of evaluation, can it make any other transition during evaluation? Why or Why not? Explain briefly, how as a VLSI designer you can optimize the performance of domino logic circuits? Illustrate a domino logic circuit. **(5)**
- b)** Explain in brief the meanings of regularity, modularity and locality with reference to VLSI design. What is hierarchy in design? **(5)**
- Q7 a)** Draw a 1 T DRAM memory cell. What are the advantages of using address multiplexing scheme in DRAM cell? What are the four key DRAM timing parameters? **(5)**
- b)** In a DRAM what is the main significance to precharge the bit-lines up to $V_{DD}/2$ instead of V_{DD} ? What are the main differences between 1-T DRAM cell and 3-T DRAM cell? **(5)**
- Q8 Write short notes on any two:** **(5 x 2)**
- a) CMOS Inverter VTC
- b) LOCOS technique
- c) BIST
- d) CMOS Implementation of SR Latch