

Registration No. :

--	--	--	--	--	--	--	--	--	--

Total number of printed pages – 3

B. Tech
PCEC 4401

Seventh Semester Back Examination – 2014

VLSI DESIGN

BRANCH (S) : AEIE, EC, ETC, IEE

QUESTION CODE : L 146

Full Marks – 70

Time : 3 Hours

Answer Question No. 1 which is compulsory and any five from the rest.

The figures in the right-hand margin indicate marks.



1. Answer the following questions :

2 × 10

- What is channel-stop implantation ?
- How Power density varies with constant voltage scaling ?
- Draw the schematic diagram of an XOR gate using CMOS Transmission gates.
- Realize AND and NAND logic using CPL.
- Draw the stick diagram of a 2-input NOR gate using CMOS technology.
- What are the stages where a VLSI chip can be tested ?
- What is Dynamic CMOS Logic ?
- What is pseudo logic circuit ?
- What is domino logic ?
- Why does CMOS dissipate power when its input changes from 1 to 0 or from 0 to 1 ?

2. (a) With the help of Band diagram, describe the operation of NMOSFET. 5

- (b) Consider the MOS structure that consists of a p-type doped silicon substrate, a silicon dioxide layer, and a metal (aluminum) gate. The equilibrium Fermi potential of the doped silicon substrate is given as $q\phi_{Fp} = 0.2$ eV. Using the electron affinity for silicon and the work function for aluminum

P.T.O.

given in Figure 1 below, calculate the built-in potential difference across the MOS system. Assume that the MOS system contains no other charges in the oxide or on the silicon-oxide interface. 5

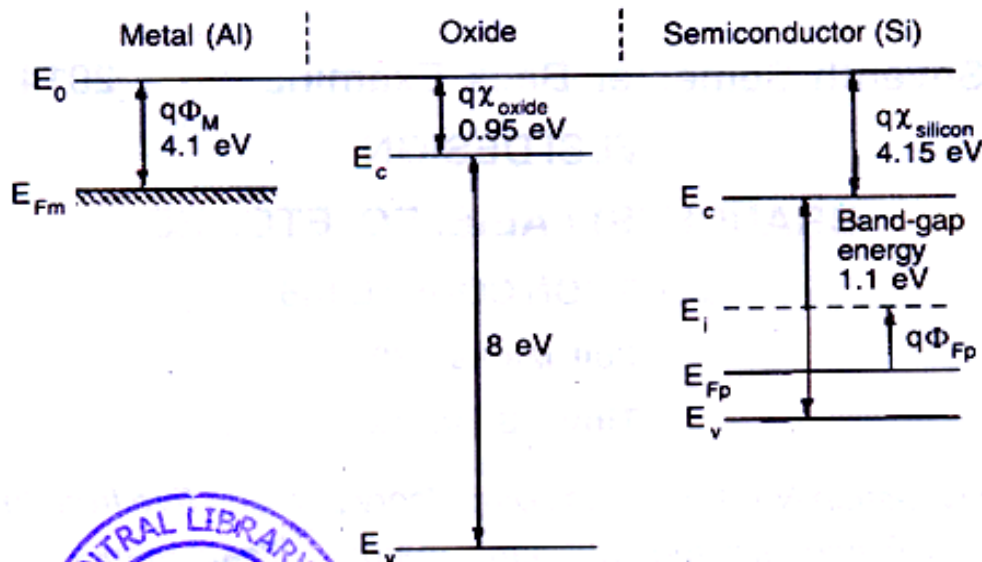


Figure 1

3. Consider the CMOS inverter circuit shown in Figure 2 below, with $V_{DD} = 3.3 \text{ V}$. The I-V characteristics of the nMOS transistor are specified as follows: when $V_{GS} = 3.3 \text{ V}$, the drain current reaches its saturation level $I_{Dsat} = 2 \text{ mA}$ for $V_{DS} = 2.5 \text{ V}$. Assume that the input signal applied to the gate is a step pulse that switches instantaneously from 0 V to 3.3 V . Using the data above, calculate the delay time necessary for the output to fall from its initial value of 3.3 V to 1.65 V , assuming an output load capacitance of 300 fF . 10

 


Figure 2

4. A company has access to a CMOS fabrication process with the device parameters listed below :

$\mu_n C_{ox} = 120 \mu A/V^2$, $\mu_p C_{ox} = 60 \mu A/V^2$, $V_{TO,n} = 0.8 V$, $V_{TO,p} = -1.0 V$, $L = 0.6 \mu m$ for both nMOS and pMOS devices and $W_{min} = 1.2 \mu m$.

Design a CMOS inverter by determining the channel widths W_n , and W_p of the nMOS and pMOS transistors, to meet the following performance specifications.

- * $V_{th} = 1.5 V$ for $VDD = 3 V$,
 - * Propagation delay times $\tau_{PHL}^* \leq 0.2 ns$ and $\tau_{PLH}^* \leq 0.15 ns$,
 - * A falling delay of 0.35 ns for an output transition from 2 V to 0.5 V, assuming a combined output load capacitance of 300 fF and ideal step input. 10
5. (a) For the Boolean expression $Y = \overline{(A + B + C)} \cdot \overline{(D + E)}$ using CMOS, find the equivalent CMOS inverter circuit for simultaneous switching of all inputs, assuming that $(W/L)_p = 15$ for all PMOS transistors and $(W/L)_n = 10$ for all NMOS transistors. 5
- (b) Implement a Full Adder circuit using CMOS. 5
6. (a) Explain how the Transmission Gate transfers both logic '0' and logic '1' efficiently. 5
- (b) Implement a 4:1 Multiplexer using Transmission Gates. 5
7. (a) Discuss about FPGA based VLSI design. 5
- (b) Describe the operation of four transistor resistive load SRAM cell. 5
8. Write short note on any **two** of the following : 5×2
- (a) Constant-Voltage Scaling
 - (b) Constant-Field Scaling
 - (c) DIBL
 - (d) HCI.

