

Registration No. : 

--	--	--	--	--	--	--	--	--	--

Total number of printed pages – 3

**B. Tech**  
**BEES 2211**

### Third Semester Regular Examination – 2014

#### NETWORK THEORY

**BRANCH(S) : AEIE, CSE, EC, EEE, ELECTRICAL, ETC, IEE, IT**

**QUESTION CODE : H 404**

Full Marks – 70

Time : 3 Hours


*Answer Question No. 1 which is compulsory and any **five** from the rest.*

*The figures in the right-hand margin indicate marks*

1. Answer the following questions :

2 × 10

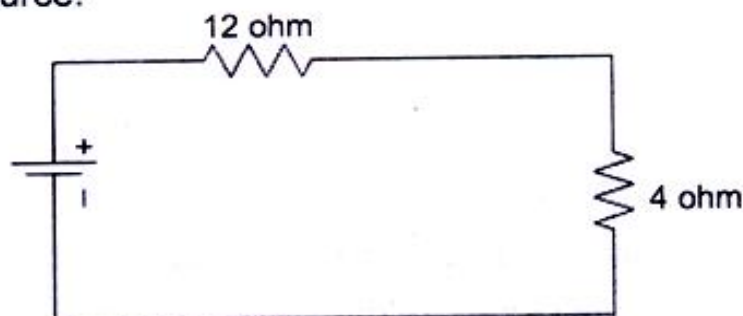- (a) Explain what is meant by duality. Give the requirement for the network to be dual of other.
- (b) Define lumped and distributed elements of a network.
- (c) Prove that efficiency under maximum power transfer condition is 50 %.
- (d) Express fourier series in exponential form and give fundamental harmonics term in fourier series.
- (e) What is the significance of time constant of R-L circuit ?
- (f) What information do poles and zeros provide in respect of network to which they relate ?
- (g) For the network shown in the following fig, convert the voltage source into current source.



**P.T.O.**

(h) A coil of resistance  $2\text{ohm}$  and inductance  $0.01\text{H}$  is connected in series with capacitor  $C$ . If maximum current occurs at  $25\text{Hz}$  find  $C$  ?

(i) Write 2 properties of Laplace transformations.

(j) Write the steps to be involved in the determination of initial conditions.

2. (a) Two generators with emfs  $200\text{V}$  and  $250\text{V}$  and armature resistance of  $2\Omega$  and  $1\Omega$  respectively are in parallel supplying a load resistance of  $10\Omega$ . Find 6

(a) current Supplied by each generator

(b) load current and


(c) load voltage.

Use super Position theorem

(b) Explain with relevant diagram, Voltage division and current division rule. 4

3. A series RLC circuit consists of  $R=100\text{ohm}$ ,  $L = 0.02\text{H}$  and  $C = 0.02\text{microfarad}$ . Calculate frequency of resonance. A variable frequency sinusoidal voltage of constant RMS value of  $50\text{V}$  is applied to the circuit. Find the frequency at which voltage across  $L$  and  $C$  is maximum. Also calculate voltage across  $L$  and  $C$  is maximum. Also calculate voltages across  $L$  and  $C$  at frequency of resonance. Find maximum current in the circuit. 10

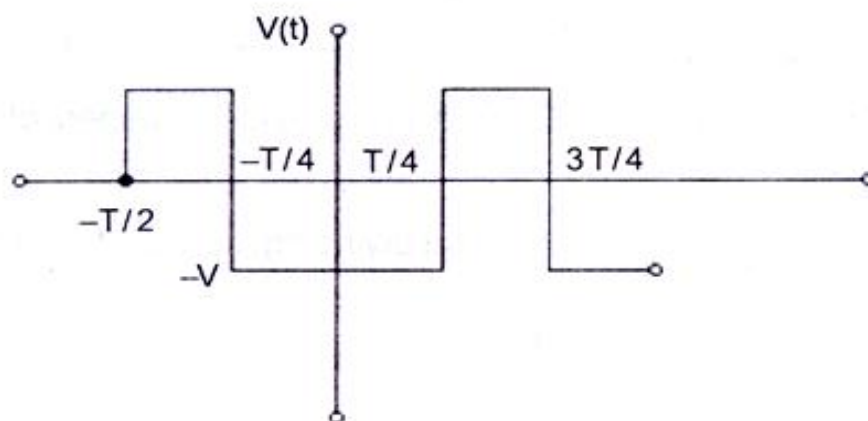
4. (a) Determine the Fourier series of the wave shown in fig. 5




(b) Find out the initial and final value of  $(s+b) / s (s+a)$ . 5

5. (a) What is the maximum possible mutual inductance of two inductively coupled coils with self inductance  $L_1=25\text{mH}$  and  $L_2=100\text{mH}$  ? 4

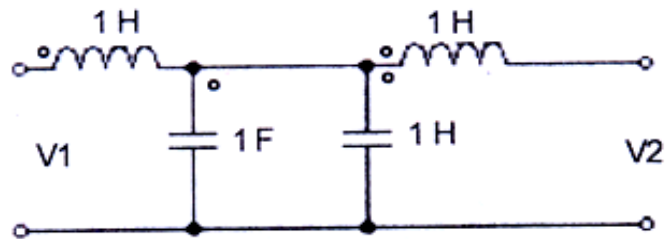- (b) Find the transfer functions  $Z_{12}(S)$  and  $G_{12}(S)$  for the network shown in fig. 6



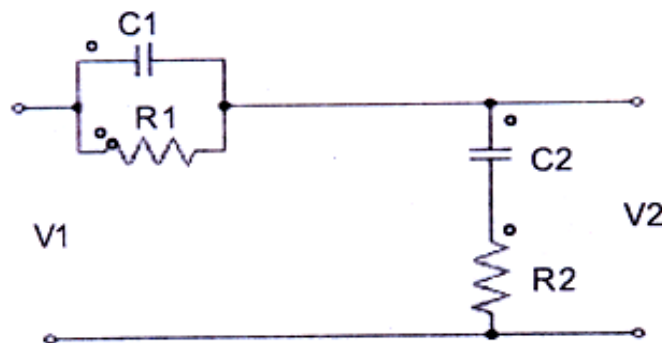6. (a) A series RLC circuit has  $Q = 75$  and a pass band (between half power Frequencies) of 160 Hz. Calculate the resonant frequency and the upper and lower frequencies of the pass band. 6
- (b) What are the various types of interconnections possible in 2 port network? 4
7. (a) For the network shown find  $G_{12}(S)$ . Write the results in the form of polynomials in  $S$  to decide poles and zeros. 5



- (b) Check the positive realness of the following function : 5

$$z(s) = \frac{s^2 + s + 6}{s^2 + s + 1}$$

8. Write short notes on any two of the following : 5 × 2
- (a) Cut-set matrix
- (b) Final value theorem
- (c) Resonance and Q factor.