

Registration No. :

--	--	--	--	--	--	--	--	--	--

Total number of printed pages – 3

B. Tech  
CPEC 5403

## Seventh Semester (Special) Examination – 2013

### VLSI DESIGN

BRANCH CODE : AEIE, EC, ETC, IEE

QUESTION CODE : 469

Full Marks – 70

Time : 3 Hours

Answer Question No. **1** which is compulsory and any **five** from the rest.

The figures in the right-hand margin indicate marks.

1. Answer the following questions : 2×10
  - (a) State the four different types of CMOS process you are familiar with.
  - (b) With a suitable diagram show the different layers in a MOS transistor.
  - (c) What is stick diagram and what are the uses of stick diagram ?
  - (d) Define threshold voltage in CMOS.
  - (e) What is channel-length modulation ?
  - (f) What are two components of power dissipation ? Explain in brief.
  - (g) What are pull-up and pull-down devices in CMOS circuits ?
  - (h) What is the structural gate-level modeling in a CAD tool like VHDL or Verilog ?
  - (i) State the different types of VLSI design styles.
  - (j) What is meant by fault models ? Give some examples of fault models.
2.
  - (a) Explain the VLSI design flow with a neat diagram. 5
  - (b) What are noise margins ? Explain how do noise margins change with increase in the p-transistor width relative to that of n-transistor. 5
3.
  - (a) Consider a non-inverting buffer shown in Figure Q3(a) below that uses an NMOS to pull up and a PMOS to pull down. The NMOS and

P.T.O.

PMOS transistors have a threshold voltage  $V_{th} = 0.2V$ . The supply voltage is  $V_{DD} = 1.2V$ . Determine the transfer characteristics and the regions of operation of the non-inverting buffer. 5

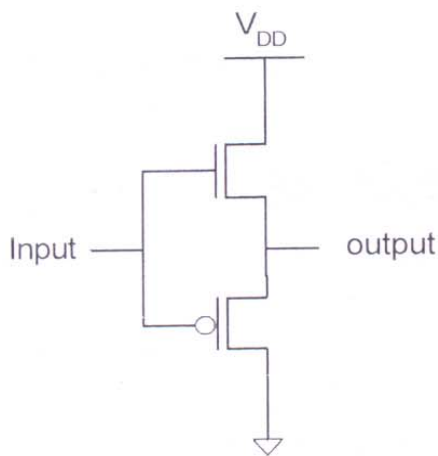


Figure Q3(a)

 


Figure Q3(b)

- (b) Why is the cross coupling and PMOS-pull-ups included in the CPL gate shown in Figure Q3(b) above? What problem are they trying to solve? 5
4. Derive the CMOS inverter DC characteristics and obtain the relationship for output voltage at different region in the transfer characteristics. 10
5. (a) Draw a transistor level schematic for a CMOS 4-input NOR gate and then sketch a stick diagram for the same. 5
- (b) For a CMOS NOR2 gate, prove that if the threshold voltages  $V_{Th,n} = |V_{Th,p}|$  and  $k_n = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_n = k_p = \frac{1}{2} \mu_p C_{ox} \left( \frac{W}{L} \right)_p$  then, the threshold voltage of the NOR gate is given by  $V_{th} (NOR2) = \frac{(V_{DD} + V_{Th,n})}{3}$ . 5
6. (a) Discuss the charge sharing problems in VLSI circuits. State various circuit techniques in domino CMOS circuits for solving charge sharing problems and explain any one of them. 5
- (b) What is pass transistor logic? Discuss its limitations and design an n-MOS pass transistor which passes weak '1' and strong '0'. 5

7. (a) Consider the two VHDL processes below. How do they differ in terms of functionality ? Be specific. 5

Program 1:

PROCESS

BEGIN

WAIT UNTIL ( Clock'EVENT AND Clock = '1' );

IF Reset = '1' THEN

Q2 <= '0';

ELSE

Q2 <= D;

END IF;

END PROCESS;

Program 2:

PROCESS (Reset, Clock)

BEGIN

IF Reset = '1' THEN

Q3 <= '0';

ELSEIF ( Clock'EVENT AND Clock = '1' ) THEN

Q3 <= D;

END IF;

END PROCESS;



- (b) Explain BIST with a neat diagram. 5
8. Write short notes any **two** of the following : 5 × 2
- (a) P-well process technology
  - (b) IDDQ testing
  - (c) CMOS D Latch
  - (d) Pass Transistor Logic.