



GIET UNIVERSITY, GUNUPUR – 765022

B. Tech (Fourth Semester – Regular) Examinations, June – 2021

BPCEC4010 – DIGITAL ELECTRONICS

(E.C.E)

Time: 2 hrs

Maximum: 50 Marks

Answer ALL Questions


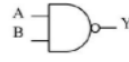

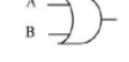
The figures in the right hand margin indicate marks.


PART – A: (Multiple Choice Questions)

(1 x 10 = 10 Marks)


Q.1. Answer ALL questions

[CO#] [PO#]

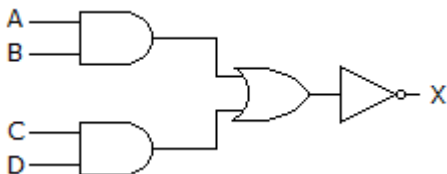
- a. Convert decimal number 255 to octal and choose the below options for appropriate answer? CO1 PO2
 (i) 263 (ii) 377
 (iii) 155 (iv) 473
- b. Convert decimal number (0.6875)₁₀ to binary and choose the below options for appropriate answer? CO1 PO3
 (i) (0.1011)₂ (ii) (0.1001)₂
 (iii) (0.1010)₂ (iv) (0.1111)₂
- c. Find the AND gate from the following? CO1 PO1
 (i)  (ii) 
 (iii)  (iv) 
- d. How many 3-line-to-8-line decoders are required for a 1-of-32 decoder? CO2 PO2
 (i) 0 (ii) 2
 (iii) 4 (iv) 6
- e. Which of the figures in figure (a to d) is equivalent to figure shown below? CO2 PO3




(i)

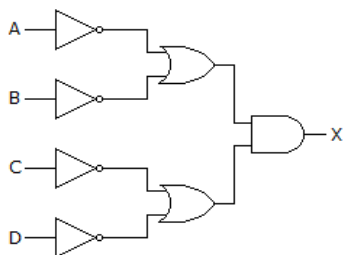


(ii)

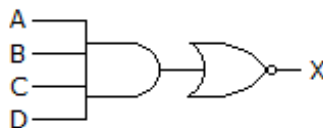

(iii)

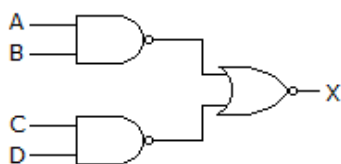

(iv)

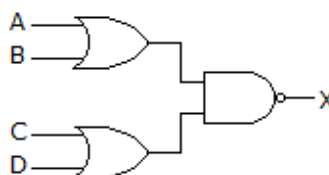

- f. Which gate is best used as a basic comparator in combinational design? CO2 PO1
 (i) AND (ii) NAND
 (iii) NOR (iv) XOR

g. The simplest register only consists of?		CO3	PO1
(i) Counter	(ii) RAM		
(iii) EPROM	(iv) Flip-Flop		
h. A decimal counter has?		CO3	PO2
(i) 5 stages	(ii) 15 stages		
(iii) 10 stages	(iv) 0 stages		
i. RTL consists of?		CO4	PO2
(i) Resistor, transistor and inductors	(ii) Resistor, diodes and BJTs		
(iii) Resistor and transistor	(iv) Resistor, capacitors and diodes		
j. Which of the following logic family has the least propagation delay?		CO4	PO1
(i) RTL	(ii) DTL		
(iii) I ² L	(iv) CMOS		

PART – B: (Short Answer Questions)

(2 x 5 = 10 Marks)

Q.2. Answer **ALL** questions

	[CO#]	[PO#]
a. If $x = 1000$ and $y = 0101$, then perform $x-y$ using 2's complement subtraction?	CO1	PO3
b. State and prove the associative law of Boolean algebra?	CO1	PO2
c. Define the Finite State Machine in logic design?	CO2	PO1
d. Explain the functioning of PIPO and PISO registers?	CO3	PO1
e. What is the importance of ADC in electronics?	CO4	PO1


PART – C: (Long Answer Questions)

(6 x 5 = 30 Marks)

Answer **ANY FIVE** questions

Marks [CO#] [PO#]

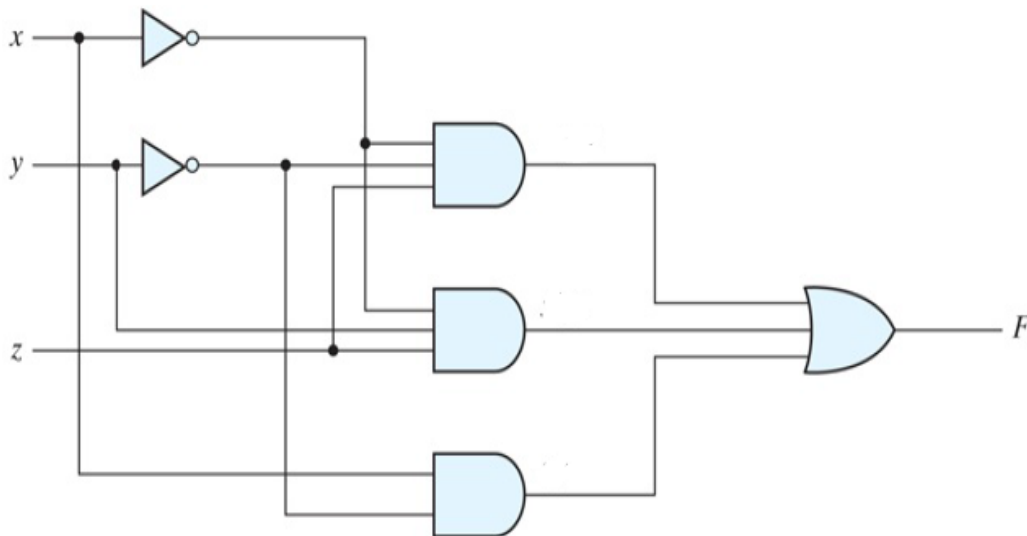3. Solve the below circuit for the function F_2 ? And find for what values of x , y and z does the value of the function will be 1?



4. Simplify the Boolean function F using K-Map and implement to the minimum logic possible? Further verify the circuit with random samples?
 $F(x, y, z) = \Sigma(2, 3, 4, 5)$
5. With a neat sketch explain how 3:8 decoder will operate?

- | | | | |
|--|-----|-----|-----|
| 6. Illustrate the functioning of Magnitude Comparator with a suitable diagram and explain its functioning? | (6) | CO2 | PO2 |
| 7. Design a 4 bit Universal Shift Register and explain its functioning? | (6) | CO3 | PO3 |
| 8. Design 1kB ROM and explain its internal logic? | (6) | CO3 | PO2 |
| 9. “Interfacing a digital computer to the analog world”, Evaluate the statement? | (6) | CO4 | PO3 |
| 10. Explain about DTL logic family in brief? | (6) | CO4 | PO2 |

--- End of Paper ---