

--	--	--	--	--	--	--	--	--	--



GIET UNIVERSITY, GUNUPUR – 765022

B. Tech (Fourth Semester – Regular) Examinations, June – 2021
BPCEL4040 / BPCEE4040 ANALOG AND DIGITAL ELECTRONIC CIRCUITS
 (Common to EE and EEE)

Time: 2 hrs

Maximum: 50 Marks

Answer ALL Questions

The figures in the right hand margin indicate marks.

PART – A: (Multiple Choice Questions)

(1 x 10 = 10 Marks)

Q.1. Answer **ALL** questions

[CO#] [PO#]

- | | | |
|---|---|---|
| a. Photodiode is used in the detection of | 1 | 1 |
| (i)visible light | | |
| (ii)Invisible light | | |
| (iii)No light | | |
| (iv)Both visible and invisible light | | |
| b. In ideal Differential Amplifier ,if same signal is given to both inputs, then output will be | 1 | 1 |
| (i)same as input | | |
| (ii)double the input | | |
| (iii)Not equal to zero | | |
| (iv)Zero | | |
| c. Which of the following material can be used to produce infrared LED? | 1 | 1 |
| (i)Si | | |
| (ii)GaAs | | |
| (iii)Cds | | |
| (iv)Pbs | | |
| d. An ideal op-amp requires infinite bandwidth because | 2 | 1 |
| (i)signal can be amplified without attenuation | | |
| (ii)output common-mode noise voltage is zero | | |
| (iii)output voltage occurs simultaneously with input voltage changes | | |
| (iv)Output can drive infinite number of devices | | |
| e. When a differential amplifier is operated single-ended, | 2 | 1 |
| (i)the output is grounded | | |
| (ii)one input is grounded and signal is applied to the other | | |
| (iii)both inputs are connected together | | |
| (iv)the output is not inverted | | |
| f. What does ASCII stand for? | 3 | 1 |
| (i)American Standard Code for Information Interchange | | |
| (ii)American Scientific Code for Information Interchange | | |
| (iii)American Scientific Code for Interchanging Information | | |
| (iv)American Standard Code for Interchanging Information | | |
| g. Which of the following combinations of logic gates can decode binary 1101? | 3 | 1 |
| (i)One 4-input AND gate | | |
| (ii)One 4-input AND gate, one inverter | | |
| (iii)One 4-input AND gate, one OR gate | | |
| (iv)One 4-input NAND gate , one inverter | | |
| h. The ALU gives the output of the operation and the output is stored in the | 3 | 1 |
| (i)Memory devices | | |
| (ii)Registers | | |
| (iii)Flags | | |
| (iv)Output unit | | |
| i. One example of the use of an S-R flip-flop is as | 4 | 1 |
| (i)Transition pulse generator | | |
| (ii)Racer | | |
| (iii)Switch debouncer | | |
| (iv)Astable oscillator | | |
| j. What is meant by the parallel load of a shift register? | 4 | 1 |

(i) All FFs are preset with data

(ii) Each FF is loaded with data, one at a time

(iii) Parallel shifting of data

(iv) All FFs are set with data

PART – B: (Short Answer Questions)

(2 x 5 = 10 Marks)

Q.2. Answer *ALL* questions

[CO#] [PO#]

- | | | |
|---|---|---|
| a. Draw a block diagram of series voltage regulator? | 1 | 1 |
| b. What is meant by quiescent point? | 1 | 1 |
| c. Write an application of monostable multivibrator | 2 | 1 |
| d. What is known as gray code and write any 2 examples of gray with decimal equivalent? | 3 | 1 |
| e. What is the use of multiplexer in combinational logic design? | 4 | 1 |

PART – C: (Long Answer Questions)

(6 x 5 = 30 Marks)

Answer *ANY FIVE* questions

Marks [CO#] [PO#]

- | | | | |
|---|-----|---|---|
| 3. Write a short notes on LED | (6) | 1 | 1 |
| 4. Write a Comparison of BJT with FET | (6) | 1 | 1 |
| 5. Explain the integrator with derivation. | (6) | 2 | 1 |
| 6. Brief notes on IC741 Specification. | (6) | 2 | 1 |
| 7. Represent the decimal number (a) 396 and (b) 4096 in binary form in
i. Binary code
ii. BCD code
iii. Excess-3 code
iv. Octal code
v. Hex code | (6) | 3 | 2 |
| 8. Simplify the following Boolean function $F(A,B,C,D) = \Sigma(0,1,2,5,8,9,10)$ in
(a) sum of product and (b) product of sums. | (6) | 3 | 2 |
| 9. Design a 3-bit synchronous counter using J-K FLIP-FLOPS | (6) | 4 | 2 |
| 10. Write a short notes on SISO, SIPO, PIPO, PISO with diagram. | (6) | 4 | 1 |

--- End of Paper ---