

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|



GIET UNIVERSITY, GUNUPUR – 765022

M. Sc (Third Semester) Examinations, December' 2020

PHPE 302 – ELECTRONICS

(Physics)

Time: 2 hrs

Maximum: 50 Marks


(The figures in the right hand margin indicate marks.)

PART - A

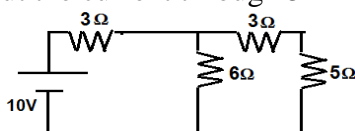Q.1. Answer ALL the Questions.

(2 x 10 = 20)

- What is the effect of negative feedback on bandwidth and voltage gain of a voltage series feedback amplifier?
- What are the advantages of crystal controlled oscillator over R-C phase shift oscillator?
- Explain the statement- “A JFET is a voltage controlled device whereas BJT is a current controlled device”.
- For a given OP AMP the CMRR is 10^5 and differential gain is 10^5 . Find the common mode gain of this OP AMP.
- Give the truth table of a J-K flip flop.
- Find out the current through $5\ \Omega$ resistor in the following circuit using Thevenin's theorem.



- Simplify the logic expression $Y = \overline{\overline{AB}} + \overline{A} + AB$
- Draw the output wave shape of an OP AMP integrator with a square-wave input.
- Why are open – loop OP AMP configurations not used in linear applications?
- What are the differences between BJT and JFET ?

PART-B

Q.3. Answer ANY FIVE Questions.

(6 x 5 = 30 Marks)

- Draw the small signal low frequency hybrid parameter equivalent circuit of a CE transistor amplifier and derive the expressions for power gain in trans conductance model.
- Write the relation between drain current and gate-to-source voltage for an enhancement type MOSFET. How is an n-channel MOSFET used as a resistor?
- What is Nyquist criterion for a regenerative circuit? Describe the physical significance of Nyquist criterion in an oscillator.
- What is meant by frequency stability of an oscillator? Why is the frequency stability of piezoelectric crystal controlled oscillator high?
- What is a non-inverting OP AMP? With a neat circuit diagram derive an expression for voltage gain, input impedance and output impedance of non-inverting amplifier using OP AMP.
- Explain how an OP AMP can be used as a voltage comparator.
- Show that a bubbled AND gate is equivalent to a NOR gate and a bubbled OR gate is equivalent to NAND gate.
- With the help of a truth table explain the operation of a J-K flip-flop having preset and clear input facilities.

- End of Paper -