

--	--	--	--	--	--	--	--	--	--



GIET UNIVERSITY, GUNUPUR – 765022
M. Tech (Third Semester – Regular) Examinations, December – 2020
MPEPE 3012 – FACTS AND CUSTOM POWER DEVICES
(Power Electronics)

Time: 2 hrs

Maximum: 50 Marks

The figures in the right hand margin indicate marks.

PART – A (2 x 10 = 20 Marks)

Q.1. Answer *ALL* questions

- a. Recall the need for variable series compensation.
- b. Identify the required inputs that correspond to three basic modes of SVC control.
- c. What do you understand by TCR?
- d. Mention the two basic approaches for controllable series compensation.
- e. Define TCSC.
- f. Pointout the importance of unified power flow controller.
- g. Appraise the term reactive power.
- h. List out the causes for harmonics and how does it affects the electrical system?
- i. How voltage sag can be mitigated?
- j. Recall any two IEEE standards on power quality.

PART – B (6 x 5 = 30 Marks)

Answer *ANY FIVE* questions

Marks

- | | |
|---|-----|
| 2. Indicate and show the transmission line compensated by controllable reactive power source at receiving end. | (6) |
| 3. Explain the operation of TSC with a series reactor. | (6) |
| 4. Elucidate SSSC with its schematic and equivalent circuit. | (6) |
| 5. With a neat sketch, illustrate the output voltage waveform of the delay angle controlled thyristor tap changer supplying a purely capacitive load. | (6) |
| 6. Enumerate GTO controlled series capacitor showing the principle of turn off delay angle control. | (6) |
| 7. Recall the equations intended for reactive power control in a three phase system with aid of Clarke's transformation. | (6) |
| 8. Draw the equivalent circuit of UPFC and assess in detail. | (6) |
| 9. Explain IPFC involving 'n' converters with a neat sketch. | (6) |

--- End of Paper ---