

--	--	--	--	--	--	--	--	--	--



GIET UNIVERSITY, GUNUPUR – 765022

M. Tech (First Semester – Regular) Examinations, June – 2021

MPEEC1042 – RF and Microwave Circuit Design

(E.C.E)

Time: 2 hrs

Maximum: 50 Marks

The figures in the right hand margin indicate marks.

PART – A

(2 x 10 = 20 Marks)

Q1. Answer **ALL** questions

- Draw the circuit model of two wire parallel transmission line with all the parameters.
- A transmission line has a characteristic impedance of $50+j0.01\Omega$ and is terminated in a load impedance of $73-j42.5\Omega$. Calculate (a) reflection coefficient (b) the VSWR.
- Describe the characteristics of the smith chart?
- Why S-parameters are popularly used in microwave frequencies?
- A 1 W power source is connected to the input of a directional coupler with $C=20\text{dB}$, directivity (D) is 25dB and an insertion loss of 0.7dB. Find the output powers in dBm at the through coupled and isolated ports. [Assume all ports to be matched]
- Define critical coupling technique in resonator circuit.
- Define power added efficiency.
- Define gain compression for a nonlinear component.
- Define third order intercept point for a nonlinear component.
- An RF input signal at 1800 MHz is down-converted in a mixer to an IF frequency of 87 MHz. What are the two possible LO frequencies?

PART – B

(6 x 5 = 30 Marks)

Answer ANY FIVE questions


Marks

- Derive the expression for input impedance of a terminated transmission line. Find out the equation short circuited transmission line. **(6)**
- A two-port network is known to have the following scattering matrix: **(6)**

$$[S] = \begin{bmatrix} 0.25\angle 0^\circ & 0.75\angle -45^\circ \\ 0.75\angle 45^\circ & 0.2\angle 0^\circ \end{bmatrix}$$

Determine the network is not reciprocal and lossless. If port 2 is terminated with a matched load, what is the return loss seen at port 1.

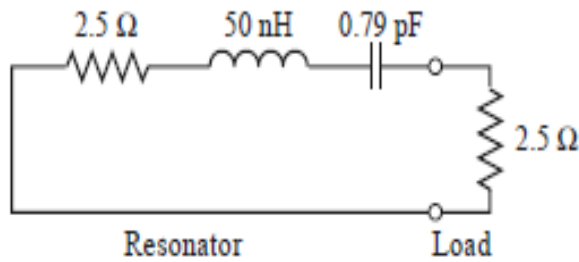- A series RLC resonator with an external load is shown below. Find the resonant frequency, the unloaded Q, and the loaded Q. **(6)**



5. Design a low-pass composite filter with a cutoff frequency of 2 MHz and impedance of 75Ω . Place the infinite attenuation pole at 2.05 MHz. (6)
6. Find the S-matrix for an ideal 3dB 90° coupler. (6)
7. Explain principles of operation of Gunn diode. (6)
8. An RF amplifier has the following parameters: $S_{11} = 0.3\angle -70^\circ$; $S_{21} = 3.5\angle 85^\circ$; $S_{12} = 0.2\angle -10^\circ$; $S_{22} = 0.4\angle -45^\circ$. Furthermore, the input side of the amplifier is connected to a voltage source with $V_s = 5\angle 0^\circ$ and source impedance $Z_s = 40\Omega$. The output is utilized to drive an antenna which has an impedance of $Z_L = 73\Omega$. Assuming that the S-parameters of the amplifier are measured with reference to a $Z_0 = 50\Omega$ characteristic impedance, find the following quantities: (a) transducer gain, available gain and operative gain (b) power delivered to the load, available power and incident power to the amplifier. (6)

--- End of Paper ---