

--	--	--	--	--	--	--	--	--	--



**GIET UNIVERSITY, GUNUPUR – 765022**  
M. Tech (First Semester – Regular) Examinations, June – 2021  
**MPEPE1033 – POWER QUALITY**  
(Power Electronics)

Time: 2 hrs

Maximum: 50 Marks

**The figures in the right hand margin indicate marks.**

**PART – A****(2 x 10 = 20 Marks)**Q1. Answer **ALL** questions

- a. Define voltage flicker according to IEEE standard 1159.
- b. Write the significance of IEEE – Std 519.
- c. Find the total harmonic distortion of a voltage waveform with the following harmonic frequency make up: fundamental = 114V, 3<sup>rd</sup> harmonic = 4V, 5<sup>th</sup> harmonic = 2V, 7<sup>th</sup> harmonic = 1.5V and 9<sup>th</sup> harmonic = 1V.
- d. What is triplex harmonics?
- e. Specify the reason for the need of shunt capacitors.
- f. List the sources power quality sources.
- g. What is the need of power quality improvement?
- h. Give the examples for passive and active filters.
- i. Write down the examples of Lyapunov function
- j. Recall the advantages of Hamilton equation.

**PART – B****(6 x 5 = 30 Marks)**Answer ANY FIVE questions**Marks**

2. A 14.4 kV three phase system serves a distribution line with an impedance of  $2+j6$  ohms. If the voltage at the sending end remains 1.4kV. Obtain the sag magnitude for the balanced three phase load of  $10+j5$  ohm per phase. **(6)**
3. Explain power quality issues occurred due to three phase power converters with suitable circuits and waveforms. **(6)**
4. Discuss the Harmonic distortion due to fluorescent lamps with help of its waveform. **(6)**
5. Demonstrate how transformers aid to improve the power quality. **(6)**
6. With the help of neat schematic diagram explain the function of Power Factor Control based on Bilateral Single Phase. **(6)**
7. Explain in detail control methods for single phase APFC. **(6)**
8. Develop the design procedure for variable structure adaptive model for any one control application. **(6)**

--- End of Paper ---