



**GIET UNIVERSITY, GUNUPUR – 765022**  
**M. Tech (Second Semester Examinations) – October' 2021**  
**MPCPE2010 – POWER ELECTRONIC CONVERTERS**  
**(Power Electronics)**

Time: 2 hrs

Maximum: 50 Marks

(The figures in the right hand margin indicate marks)

**PART – A**Q.1. Answer **ALL** questions

(2 x 10 = 20)

- What is meant by delay angle?
- A single-pulse transformer with secondary voltage of 230 V, 50 Hz, delivers power to bulb of  $R = 10 \Omega$  through a half-wave controlled rectifier circuit. For  $\alpha = 60^\circ$ , find the average current in the bulb.
- Can you overcharge a 12-volt battery? Justify.
- What are the applications of dc chopper?
- A step down chopper is operated at 240V at duty cycle of 75%. Find the value of RMS switch (IGBT/MOSFET) current. Take  $R = 10 \Omega$ .
- Why thyristors are not preferred for inverters?
- A single phase full bridge inverter has load  $R = 2 \Omega$ , and dc voltage source  $V_s = 230$  V. Find the rms value of the fundamental load current.
- Compare CSI and VSI.
- What is meant by Cyclo-converter?
- What are the disadvantages of continuous gating signal?


**PART – B**

(6 x 5 = 30 Marks)

Answer **ANY FIVE** questions

Marks

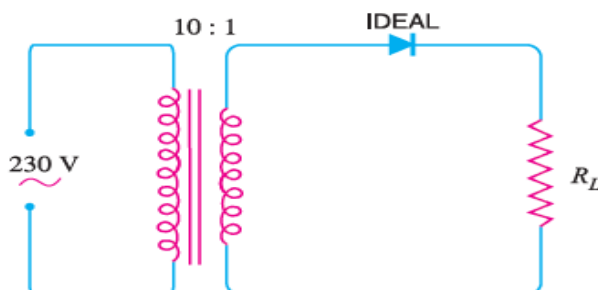- Draw and explain the single phase half controlled converter operation with RL load and derive the average value of output voltage and power factor. (6)
- An AC supply of 230 V is applied to a half-wave rectifier circuit through a transformer of turn ratio 10: 1. Find (i) the output DC voltage and (ii) the peak inverse voltage. Assume the diode to be ideal. (6)



- Describe the working principle of buck converter with relevant waveform. (6)
- Explain the operation of single phase VSI Full Bridge with R Load. (6)
- Explain the following PWM techniques used in inverter. (6)
  - Sinusoidal PWM
  - Multiple PWM.

7. Explain the operation of single phase AC voltage controller with RL load. (6)
8. A single phase voltage controller feeds power to a resistive load of  $3\Omega$  from 230V, 50 Hz source. Calculate the maximum values of average and RMS thyristor currents for any firing angle? (6)

--- End of Paper ---