



GIET UNIVERSITY, GUNUPUR – 765022

B. Tech (Third Semester - Regular) Examinations, December – 2022
21BECPC23001 – Analog Electronic Circuits
 (ECE)

Time: 3 hrs

Maximum: 70 Marks

Answer ALL questions

(The figures in the right hand margin indicate marks)

PART – A

(2 x 5 = 10 Marks)

Q.1. Answer **ALL** questions

	CO #	Blooms Level
a. Why BJT is a current-controlled device whereas FET is a voltage-controlled device?	CO-1	K1
b. Determine the value of g_m of JFET.	CO-2	K3
c. What do you mean by slew rate of an OPAMP?	CO-1	K1
d. Neatly sketch and label DC load line of an Emitter stabilized bias circuit with $V_{CC} = 12V$, $R_C = 1.5 K\Omega$, $R_E = 1.8 K\Omega$, $R_B = 82 K\Omega$.	CO-2	K2
e. Draw the drain and transfer V-I characteristic of N-Channel JFET.	CO-3	K1

PART – B

(15 x 4 = 60 Marks)

Answer **ALL** the questions

	Marks	CO #	Blooms Level
2. a. Define biasing of BJT and explain need for biasing.	8	CO-1	K1
b. For a Emitter Stabilized bias circuit with $V_{CC} = 16V$, $R_B = 470 K\Omega$, $R_C = 2.7 K\Omega$, $\beta = 90$. Determine: i) $S(I_{CO})$ ii) $S(V_{BE})$ iii) $S(\beta)$ using β (T1) as specified in the diagram and β (T2) as 25% more. iv) Determine the net change in I_C if a change in operating conditions results in I_{CO} increasing from 0.2 to 10 V_{BE} drops from 0.7 to 0.5 V, and increases 25%.	7	CO-1	K2
(OR)			
c. Draw the circuit of voltage divider bias. Take the circuit parameter as, $V_{CC} = 10V$, $R_2 = 17K\Omega$, $R_1 = 83K\Omega$, $R_C = 2K\Omega$, $R_E = 0.5K\Omega$, find I_B , I_C , V_{CE} , V_C , V_E . The transistor has $\beta=100$ and $V_{BE} = 0.7V$.	8	CO-3	K2
d. Explain the self-biasing of a JFET.	7	CO-3	K2
3.a. Show that the trans-conductance g_m of a JFET is related to the drain current I_{DS} given by $g_m = \frac{2}{ V_P } \sqrt{I_{DSS} I_{DS}}$ where the symbols have their usual meanings	8	CO-2	K3
b. Determine the following for the voltage divider biasing of JFET (i) IDQ and V_{GSQ} . (ii) VD . (iii) VS . (iv) VDS . If $R_1 = 2.1M\Omega$, $R_2 = 270K\Omega$, $R_D = 2.4 K\Omega$, $R_S = 1.5 K\Omega$, $I_{DSS} = 8mA$, $V_P = -4V$.	7	CO-2	K1
(OR)			
c. Draw an emitter follower circuit. Draw its r_e equivalent circuit. Derive its voltage gain.	8	CO-1	K2
d. Draw the ac equivalent circuit for self-bias configuration $V_{GS} = 2.6 V$ and $I_D = 2.6 mA$, with $I_{DSS} = 8 mA$ and $V_P = 6 V$. (i) Determine g_m . (ii) Find Z_i (iii) Calculate Z_o . (iv) Calculate A_v .	7	CO-3	K1
4.a. Design a OPAMP based analog circuits which will give an output voltage, $V_o = 0.5 V_1 - 2 V_2 + 0.25 V_3$, where V_1 , V_2 and V_3 are three input voltages.	8	CO-2	K1
b. Write short notes on integrator and differentiator using Op-Amp.	7	CO-3	K1

(OR)

- | | | | |
|--|---|------|----|
| c. Derive the conditions of oscillation in a Wein-bridge oscillator. | 8 | CO-1 | K1 |
| d. Derive the conditions for oscillation in a RC phase shift oscillator. What type of waveform does it generate? | 7 | CO-1 | K1 |
| 5.a. List the characteristics of an ideal op-amp. Draw the equivalent circuit diagram. | 8 | CO-1 | K2 |
| b. Derive an expression for the voltage gain of an instrumentation amplifier. What are its applications? | 7 | CO-2 | K1 |

(OR)

- | | | | |
|---|---|------|----|
| c. Explain the concept of negative feedback. Also derive a term for gain with feedback. | 8 | CO-3 | K2 |
| d. Draw a neat circuit diagram of push pull class B amplifier. Explain its working | 7 | CO-2 | K1 |

--- End of Paper ---