

--	--	--	--	--	--	--	--	--	--



GIET UNIVERSITY, GUNUPUR – 765022

B. Tech (Third Semester - Regular) Examinations, December – 2022
21BECPC23002 - Electrical and Electronic Measurements
 (ECE)

Time: 3 hrs

Maximum: 70 Marks

Answer ALL questions

(The figures in the right-hand margin indicate marks)

PART – A

(2 x 5 = 10 Marks)

Q.1. Answer **ALL** questions

	CO #	Blooms Level
a. Determine the resolution of a moving coil voltmeter having a uniform scale with 50 divisions; the full-scale reading is 50 V and $1/10^{th}$ of a scale division can be estimated with a fair degree of certainty.	CO1	4
b. Derive the balance condition of Wheatstone Bridge.	CO2	3
c. Name the four intrinsic constants of a galvanometer.	CO3	2
d. Mention the various types of error in wattmeters.	CO1	2
e. What is the main cause of harmonic distortion?	CO4	1

PART – B

(15 x 4 = 60 Marks)

Answer ALL questions

	Marks	CO #	Blooms Level
2. a. Describe the working principle of a Ballistic galvanometer with a necessary diagram.	8	CO1	2
b. Explain briefly the terms: (i) Static error (ii) Sensitivity (iii) Hysteresis (iv) Drift (v) Accuracy (vi) Repeatability (vii) Linearity	7	CO3	2
(OR)			
c. Discuss the construction and principle of Electrical Resonance type frequency meter.	8	CO2	3
d. Explain errors of current and potential transformer.	7	CO3	2
3.a. Describe the loss of charge method for the determination of high resistance.	8	CO1	2
b. Explain the construction and working of a simple D.C potentiometer.	7	CO4	1
(OR)			
c. Explain with a neat sketch, construction and operation of power-factor meter.	8	CO2	3
d. Draw the block diagram of Real Time Spectrum Analyzer. Explain.	7	CO3	2
4.a. A resistance of approximate value of 80Ω is to be measured by voltmeter – ammeter method using a 1 A ammeter having a resistance of 2Ω and a 50 V voltmeter having a resistance of $5 k\Omega$.	8	CO1	2

i. Suggest which one of the two methods should be used.

ii. Suppose in the suggested method the following measurements are made:

$$I = 0.42 \text{ A}$$

&

$$V = 35.5 \text{ V}$$

What is the resulting error if the accuracy of the instruments is $\pm 0.5\%$ at full scale and the errors are standard deviations.

- b. Derive the torque equation of PMMC instrument with a suitable constructional diagram. 7 CO4 1
- (OR)
- c. A 3-phase, 10 kVA load has a PF of 0.342. The power is measured by two wattmeter method. Find the reading of each wattmeter when the PF is (i) Lagging and (ii) Leading 8 CO2 3
- d. Explain the working of a superheterodyne wave analyser. 7 CO3 2
- 5.a. Derive the relationship between capacitance and resistance using Schering Bridge. 8 CO2 3
- b. What is essential difference between a moving coil and a moving iron instrument. List the errors with the methods of compensation. 7 CO4 1
- (OR)
- c. Explain single phase induction type energy meters with its source of errors. 8 CO2 3
- d. Discuss the circuit diagram of basic wave analyser. 7 CO3 2

--- End of Paper ---