



## GIET UNIVERSITY, GUNUPUR – 765022

B. Tech (Third Semester - Regular) Examinations, December – 2022

### 21BECPC23003 / 21BELPC23002 / 21BEEPC23002 – NETWORK THEORY (ECE, EE & EEE)

Time: 3 hrs

Maximum: 70 Marks

**Answer ALL questions**


(The figures in the right hand margin indicate marks)

#### PART – A

(2 x 5 = 10 Marks)

Q.1. Answer *ALL* questionsCO # Blooms  
Level

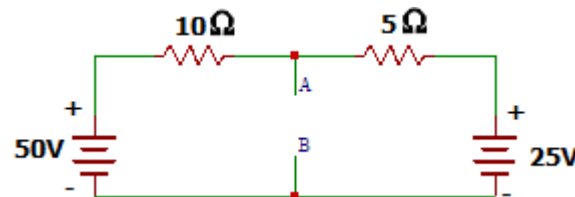- a. State the theorem on laws of conservation of energy? CO4 2
- b. Determine the equivalent Thevenin's resistance between terminals A and B in the circuit shown below. CO1 3



- c. What is Hurwitz criterion of stability of network function? CO4 2
- d. If the value of resonant frequency is 50 kHz in a series RLC circuit along with the bandwidth of about 1 kHz, then what would be the value of quality factor? CO2 3
- e. If z-parameters are  $z_{11} = 40$ ,  $z_{22} = 50$  and  $z_{12} = z_{21} = 20$ , what would be the value of  $y_{22}$ . CO3 3


#### PART – B

(15 x 4 = 60 Marks)

Answer ALL the questions

Marks CO # Blooms  
Level

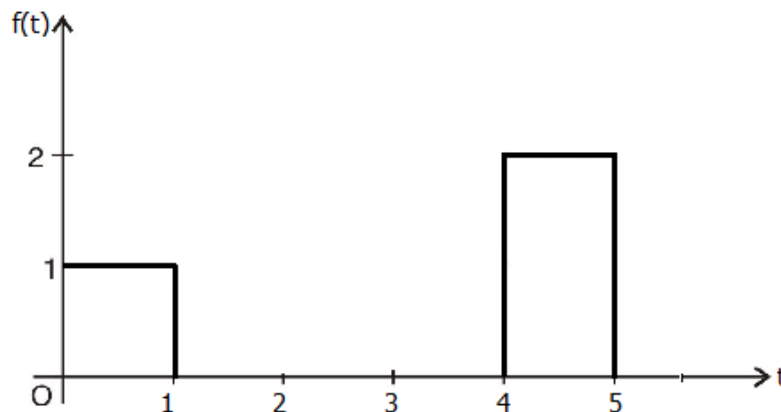
2. a. Determine the Laplace transform of the waveform shown in figure. 8 CO4 3




- b. A pure inductance of 150 mH is connected in parallel with a 40  $\mu$ F capacitor across a 50 V, variable frequency supply. Determine (a) the resonant frequency of the circuit and (b) the current circulating in the capacitor and inductance at resonance. 7 CO2 2

(OR)

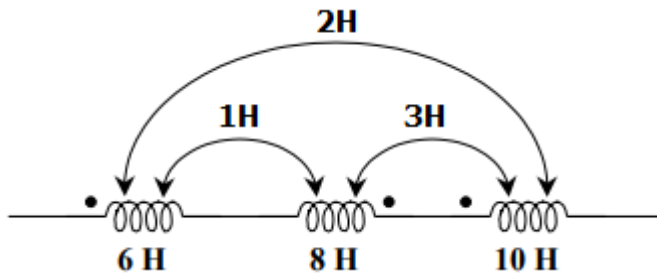
- c. For three coupled coils shown in figure. Calculate the total inductance. 8 CO2 3



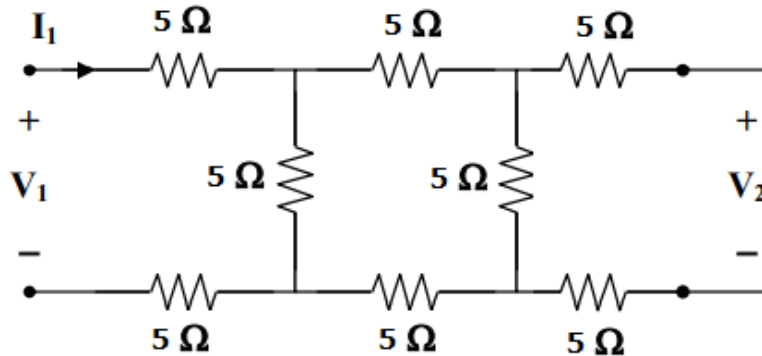- d. State and explain Reciprocity theorem with examples. What are the limitations of this theorem? 7 CO1 2
- 3.a. Find out impedance parameter of two port network. 8 CO3 3




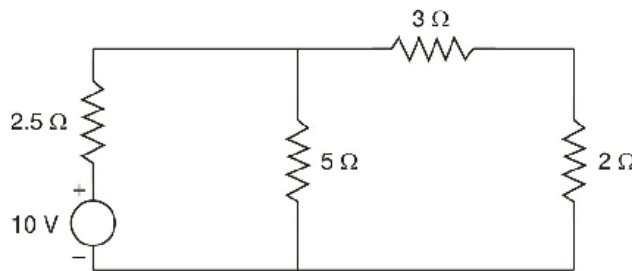- b. For the circuit shown in figure, the resistance of  $5\Omega$  changes to  $2\Omega$ . Calculate the compensation source and verify the results. 7 CO1 3



(OR)

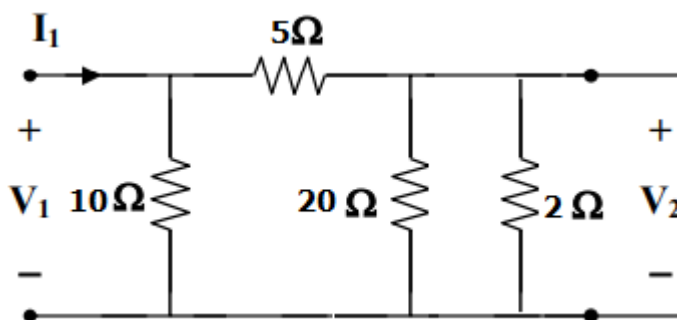
- c. What is Initial & final value theorem. Find initial value & final value of the transfer function  $F(s) = \frac{2(s+1)}{s(s+2)(s+4)}$  8 CO4 2
- d. State and explain maximum power transfer theorem. 7 CO1 2
- 4.a. Determine short circuit parameters for the network shown in figure. 8 CO3 3




- b. Explain restrictions of pole & zero on location of driving point impedance function. 7 CO4 2

(OR)

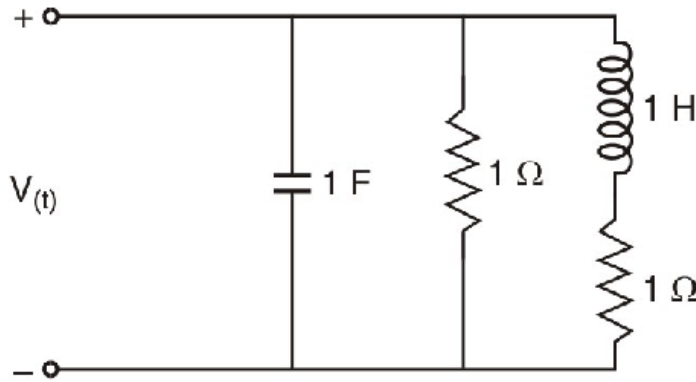- c. Determine the driving point admittance  $Y(s)$  for the network shown in figure. Draw pole zero plot. 8 CO4 3



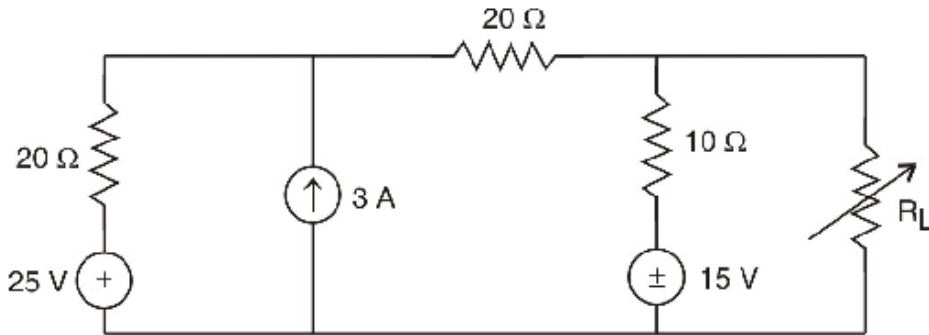- d. A series RLC circuit is resonant at 1 Megacycle/sec. its bandwidth is 5000cps & input impedance at resonance is 50 ohms. Find values of R,L,C. 7 CO2 2
- 5.a. Determine  $R_L$  for maximum power absorbing from the source and also obtain maximum power for the circuit shown in figure. 8 CO1 2




- b. Check whether the polynomial is Hurwitz or not. 7 CO4 3


$$F(s) = s^4 + s^3 + 6s^2 + 3s + 6$$

(OR)

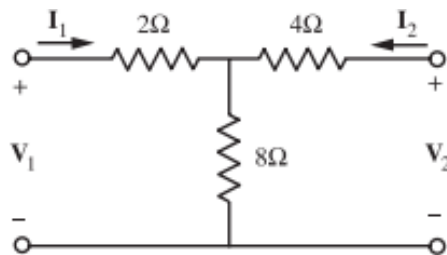- c. Find the hybrid parameter of two port network shown in figure. 8 CO3 3



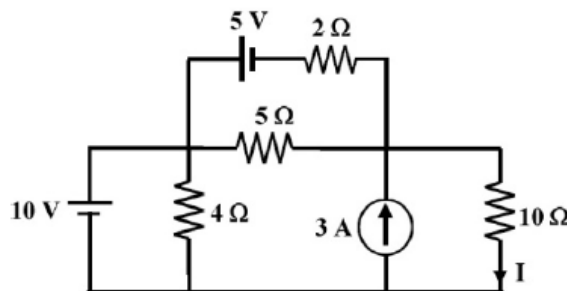- d. Find the current  $I$  using superposition theorem. 7 CO1 2



--- End of Paper ---