

--	--	--	--	--	--	--	--	--	--



GIET UNIVERSITY, GUNUPUR – 765022
 B. Tech (Third Semester - Regular) Examinations, December – 2022
21BELPC23001/21BEEPC23001– Electrical Machines – I
 (EE & EEE)

Time: 3 hrs

Maximum: 70 Marks

Answer ALL questions
(The figures in the right hand margin indicate marks)

PART – A**(2 x 5 = 10 Marks)**Q.1. Answer *ALL* questions

	CO #	Blooms Level
a. Explain the function of Commutator in a DC machine?	CO 1	1
b. What is the use of laminated armature?	CO 1	1
c. Draw the circuit diagram of DC shunt motor and identify the currents in it?	CO 2	2
d. Write any two differences of practical transformer and ideal transformer?	CO 3	2
e. What is Transformation Ratio?	CO 4	2

PART – B**(15 x 4 = 60 Marks)**Answer *ALL* the questions

	Marks	CO #	Blooms Level
2. a. Derive the EMF equation of DC machine	8	CO 1	2
b. A 4 pole lap wound DC shunt generator has a useful flux /pole 0.06 wb and number of conductors are 500. The armature resistance is 0.0375 ohm. Calculate the terminal voltage when running at 1500 rpm. If armature current is 40 A.	7	CO 1	3
(OR)			
c. Explain about the working of 3-point starter	8	CO 1	2
d. What is the significance of residual magnetism? Explain the experimental determination of OCC?	7	CO 1	2
3.a. Explain the operation of DC motor with neat diagram?	8	CO 2	2
b. A 6-pole lap connected 200 V shunt motor has 400 armature conductors. It takes 41 A on full load. The flux per pole is 0.05 wb. The armature and field resistances are 0.1 ohm and 200 ohms respectively. Contact drop per brush = 1V. Determine the speed of the motor at full load.	7	CO 2	3
(OR)			
c. Explain the methods of speed control of DC motor	8	CO 2	3
d. Explain the causes for failure to self-excitation of a DC machine with its remedial measures?	7	CO 2	2
4.a. Enumerate the differences between Auto Transformer with Two Winding Transformer	8	CO 3	2
b. A 40 KVA, 1000/100V, single phase, 50Hz transformer has a primary resistance of 4.5 ohm and reactance of 6.5ohm. The secondary resistance and reactance are 0.025ohm and 0.04ohm respectively. Find Equivalent resistance, reactance and impedance referred to secondary.	7	CO 3	3

(OR)

- c. A 4KVA, 400/200V, 50 Hz single-phase transformer has the following test data:
- OC test (LV side): 200V, 1A, 64W
- SC test (HV side): 15V, 10A, 80W
- 8 CO 3 3
- Determine equivalent circuit referred to primary side
- d. For the above problem (4C) find the efficiency of the transformer at 0.8 pf lagging.
- 7 CO 3 3
- 5.a. Derive the EMF equation of a Transformer
- 8 CO 3 2
- b. A 40 KVA, single phase transformer has 400 turns on the Primary and 100 turns on the secondary. The primary is connected to 2000V, 50Hz supply. Determine
- i) the secondary voltage on open circuit. ii) The maximum value of flux
- 7 CO 3 3
- (OR)
- c. Explain the differences between Shell type transformer and core type transformer
- 8 CO 4 2
- d. Explain the constructional features of 3-phase transformer with its advantages and disadvantages.
- 7 CO 4 2

--- End of Paper ---