



GIET UNIVERSITY, GUNUPUR - 765022

B. Tech (Third Semester Regular) Examinations, December - 2023

22BELPC23002 / 22BEEPC23002 - Network Theory

(EE & EEE)

Time: 3 hrs

Maximum: 70 Marks

(The figures in the right hand margin indicate marks)

PART - A

(2 x 5 = 10 Marks)

Q.1. Answer **ALL** questions

- | | CO # | Blooms Level |
|--|------|--------------|
| a. A resistor of 3 kΩ, a 0.05 μF capacitor, and a 120 mH coil are in series across a 5 kHz, 20 V ac source. What is the impedance expressed in polar form? | CO2 | K3 |
| b. Write some applications of maximum power transfer theorem. | CO1 | K4 |
| c. A two-port device is defined by the following pair of equations $I_1 = 5V_1 + 2V_2$, $I_2 = 3V_1 + 4V_2$. Write its impedances parameter Y11. | CO3 | K2 |
| d. Explain why the voltage across a capacitor cannot change instantaneously. | CO4 | K3 |
| e. Test the positive realness. | CO2 | K3 |

$$F(s) = \frac{s^2 + 8s + 5}{s + 2}$$


PART - B

(15 x 4 = 60 Marks)

Answer **ALL** questions

2. a. Calculate the current through 10Ω and voltage drop across it for the circuit shown in fig by using Millman's Theorem.

Marks	CO #	Blooms Level
7	CO1	K3

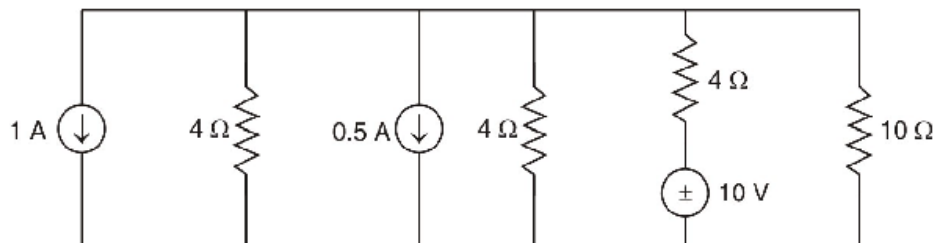


- b. A pure inductance of 150 mH is connected in parallel with a 40 μF capacitor across a 50 V, variable frequency supply. Determine (i) the resonant frequency of the circuit and (ii) the current circulating in the capacitor and inductance at resonance.

8	CO2	K2
---	-----	----

(OR)

- c. Determine the maximum power that can be delivered to the variable resistor R.

7	CO1	K3
---	-----	----

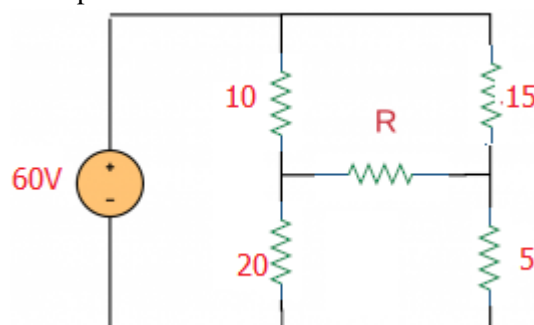


d. Find the current I using superposition theorem.

8

CO1

K2

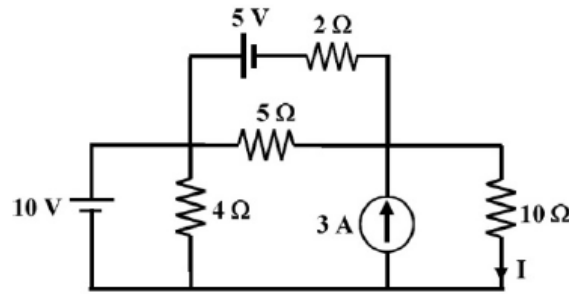


3.a. If two of such 2-port networks shown in figure are connected in series find the Z parameters of the equivalent circuit.

7

CO3

K3

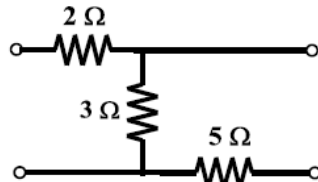

b. Obtain Y- and h- parameter, if the other parameters are given below: A=2, B= -1, C=3, and D= -2.

8

CO3

K3


(OR)

c. Find the hybrid parameter of two port network shown in figure.

7

CO3

K3

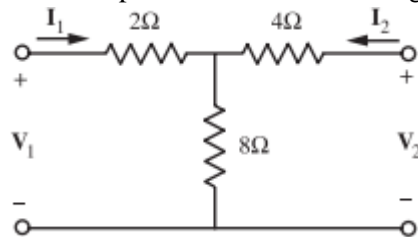

d. For a 2-port network express ABCD parameter in terms of Y Parameter.

8

CO3

K3

4.a. What is Initial & final value theorem. Find initial value & final value of the transfer function $F(s) = \frac{2(s+1)}{s(s+2)(s+4)}$

8

CO4


K2

b. Find voltage transfer function and driving point impedance of the network shown in figure.

7

CO4

K3

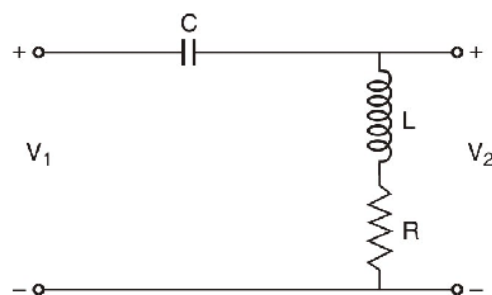

(OR)

c. Explain restrictions of pole & zero on location of driving point impedance function.

8

CO4


K2

d. Determine the Laplace transform of the waveform shown in figure.

7

CO4

K3

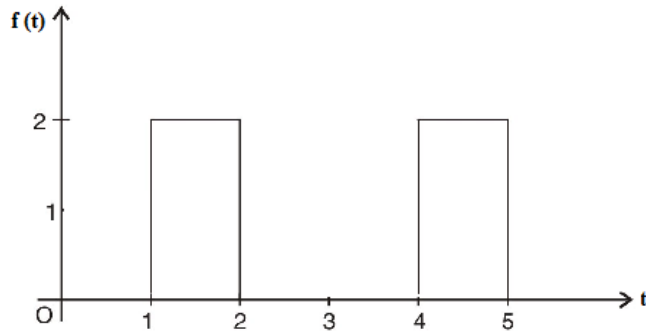


5.a. Determine the Fourier transform of one cycle of sine wave, $f(t) = A \sin \omega_0 t$.

7

CO1

K3

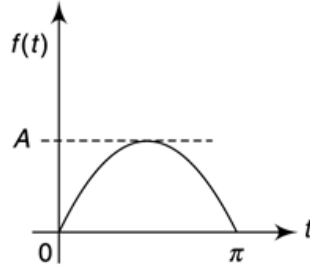

b. Realise the network by using Cauer 1st form of realisation for the function

8

CO4

K3

$$Z(s) = \frac{8s^5 + 5s^3 + 3s}{s^4 + 3s^2 + 1}$$


(OR)

c. Determine the Fourier series of the wave shown in figure.

7

CO5

K3

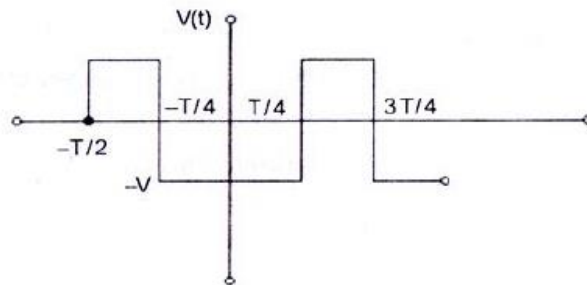

d. Obtain Cauer-1 form of realisation of the following impedance function

8

CO4

K3

$$Z(s) = \frac{s^5 + 3s^3 + s}{s^4 + 5s^2 + 4}$$

--- End of Paper ---