



GIET UNIVERSITY, GUNUPUR – 765022
 B. Tech (Third Semester Regular) Examinations, December – 2023
21BCSES23004 – Digital Electronics
 (CSE, CSE(AIML), CSE(DS))

Time: 3 hrs

Maximum: 70 Marks

Answer all questions
(The figures in the right hand margin indicate marks)

PART – A**(2 x 5 = 10 Marks)**

- | Q.1. Answer <i>ALL</i> questions | CO # | Blooms
Level |
|--------------------------------------------------------------------------------------------------------------------------------------------|------|-----------------|
| a. Convert $(597)_{10}$ to BCD code. | CO1 | K2 |
| b. Show that the dual of the exclusive-OR is equal to its complement. | CO1 | K1 |
| c. Consider the function $f(x, y, z) = \sum(2, 3, 4, 6, 7)$. Derive the canonical sum of products for the function using minterm. | CO2 | K2 |
| d. What do you mean by sequential circuit? Hence distinguish between synchronous sequential circuits and asynchronous sequential circuits. | CO3 | K2 |
| e. How many $16K \times 1$ RAMs are required to obtain a memory with a word capacity of $64K$? The word length is eight bits. | CO4 | K3 |


PART – B**(15 x 4 = 60 Marks)**Answer *ALL* questionsMarks CO # Blooms
Level

- | | | | |
|-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|----|-----|----|
| 2. a. Construct logic circuit using AND, OR, and NOT gate for the following Boolean function:
(i) $Y = (A + B)(A' + B')$
(ii) $Y = (A + B)(C' + D')(A' + C)$ | 8 | CO2 | K3 |
| b. Subtract 101011_2 from 111001_2 using 1's complement and 2's complement methods. | 7 | CO1 | K3 |
| (OR) | | | |
| c. <u>Apply DeMorgan's theorem</u> to prove that
$\overline{AB} + \overline{CD} + EF = (\overline{A} + B)(C + \overline{D})(\overline{E} + \overline{F})$
Draw the corresponding logic circuit. | 8 | CO2 | K3 |
| d. Carry out the following additions:
(i) $(+13, -11)$ using 1's complement notation.
(ii) $(-15, +9)$ using 2's complement notation. | 7 | CO1 | K3 |
| 3.a. Simplify the following Boolean function using K-map:
$F(A, B, C, D) = \sum(4, 5, 6, 7, 12, 13, 14)$
and then, write the simplified function in SoP and PoS form. | 10 | CO2 | K3 |
| b. Implement the Boolean function $F(x, y, z) = \sum(1, 2, 6, 7)$ with a multiplexer. | 5 | CO2 | K3 |
| (OR) | | | |
| c. What is a full adder circuit? Draw its truth table. Design a full adder circuit using two half adder circuits and an 'OR' gate. | 10 | CO2 | K3 |


- d. Implement the following Boolean function with a multiplexer. 5 CO2 K3
 $F(A, B, C, D) = \sum(1, 3, 4, 11, 12, 13, 14, 15)$
- 4.a. Draw the circuit diagram of a 2-bit by 2-bit binary multiplier using half-adders and logic gates. Explain its operation. 8 CO2 K3
- b. A *PN* flip-flop has four operations: no change, clear to '0', set '1', and complement; when inputs *P* and *N* are 00, 01, 10, and 11 respectively. Write the excitation table and characteristics equation of the *PN* flip-flop and realize the flip-flop using logic gates. 7 CO3 K3

(OR)

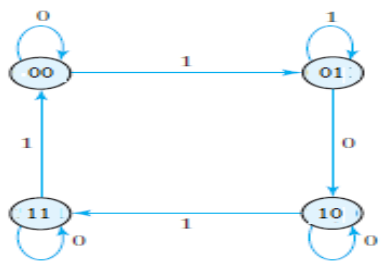- c. A magnitude comparator is a combinational circuit that compares two numbers *A* and *B*, and determines their relative magnitudes. The outcome of the comparison is specified by three binary variables that indicate whether $A > B$, $A = B$ or $A < B$. Determine the algorithm to implement this comparator and draw a 2-bit magnitude comparator using the combinational circuit. 8 CO2 K3
- d. Describe the construction and operation of a master-slave flip-flop. 7 CO3 K3
- 5.a. Design the sequential circuit specified by the state diagram of the figure using *JK* flip-flops. 10 CO3 K3



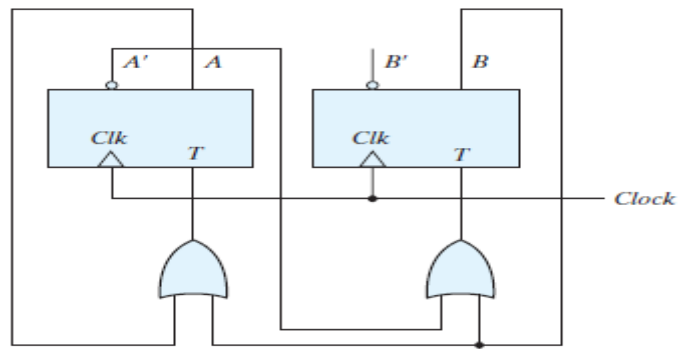- b. Design a combinational circuit using a ROM that accepts 3-input and produces its 1's complement as output. 5 CO4 K3
- (OR)
- c. Derive the state table and the state diagram of the sequential circuit shown in the figure. 10 CO3 K3



- d. Design a combinational circuit using a ROM. The circuit accepts a 3-bit binary number and generates an output binary number equal to the square of the input number. 5 CO4 K3

-- End of Paper ---