



GIET UNIVERSITY, GUNUPUR - 765022
 B. Tech (Fourth Semester - Regular) Examinations, May - 2024
22BELPC24004 - Analog and Digital Circuits
 (EE & EEE)

Time: 3 hrs

Maximum: 70 Marks

(The figures in the right hand margin indicate marks)

PART - A

(2 x 5 = 10 Marks)

Q.1. Answer **ALL** questions


- | | CO # | Blooms Level |
|--|------|--------------|
| a. A transistor has β of 100 and a base current, I_B , of $10 \mu A$. find the collector current, I_C . | CO1 | K3 |
| b. Mention some of the linear applications of op – amps | CO2 | K4 |
| c. Which gates are called as the universal gates? What are its advantages? | CO3 | K3 |
| d. Reduce $A'B'C' + A'BC' + A'BC$ | CO3 | K3 |
| e. Differentiate between latches and flip-flop. | CO4 | K4 |

PART - B

(15 x 4 = 60 Marks)


Answer **ANY FIVE** the questions

- | | Marks | CO # | Blooms Level |
|-------|-------|------|--------------|
| 2. a. | 7 | CO1 | K3 |

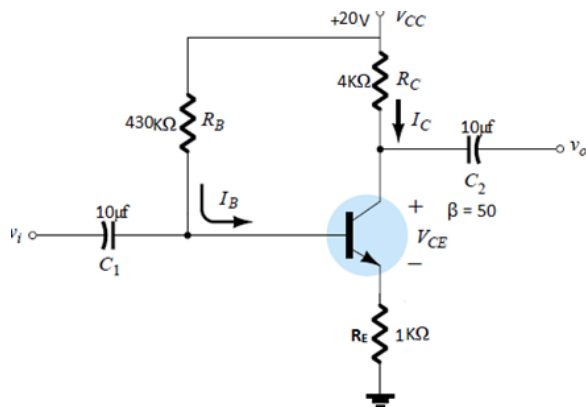


For the emitter bias network of Fig., determine

- | | | | |
|---|---|-----|----|
| b. Determine the quiescent levels of I_{CQ} and V_{CEQ} for the network of Fig. | 8 | CO1 | K3 |
|---|---|-----|----|

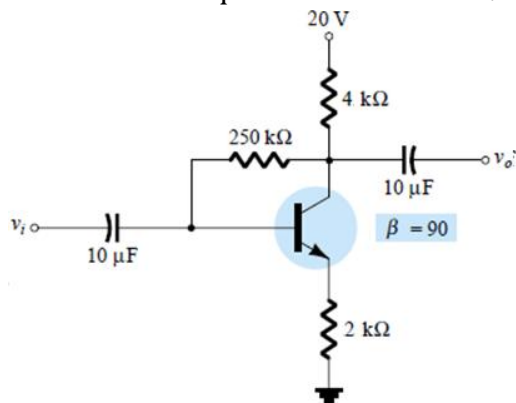


(OR)

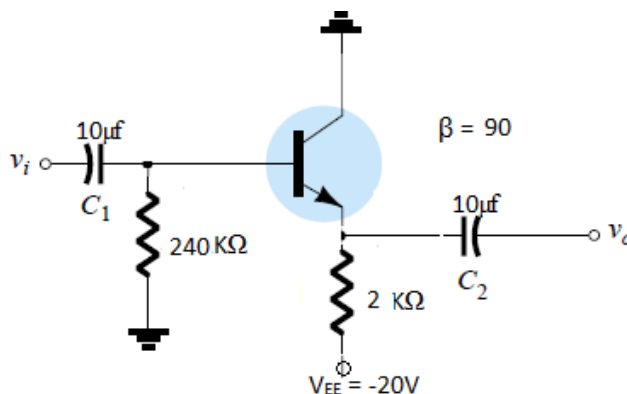
- c. Determine V_{CEQ} and I_E for the network of Fig. 7 CO1 K3



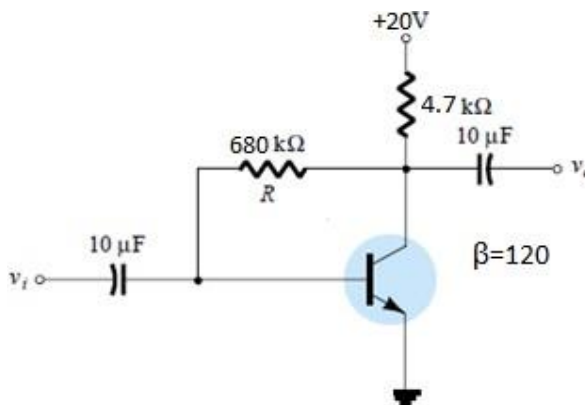- d. For the network of Fig. 8 CO1 K3
 (i) Determine I_{CQ} and V_{CEQ} .
 (ii) Find V_B , V_C , V_E , and V_{BC}



- 3.a. 7 CO2 K3

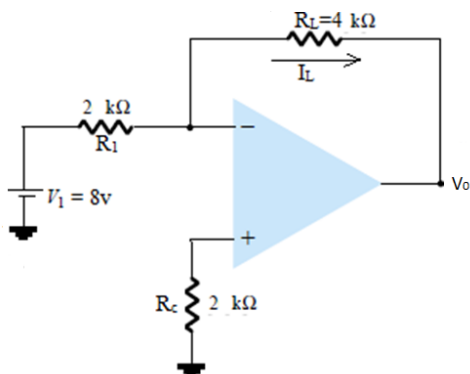


For the circuit of Fig. calculate I_L & V_0

- b. Derive the formula for gain of inverting op-amp and find the output voltage for the circuit has $R_1 = 100 \text{ k}\Omega$ and $R_f = 500 \text{ k}\Omega$, an input of $V_1 = 2 \text{ V}$? 8 CO2 K4

(OR)

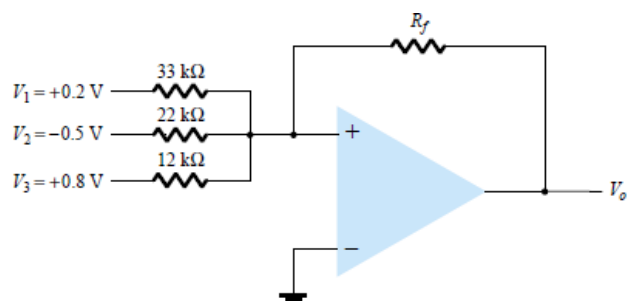- c. Calculate the output voltage developed by the circuit of Fig. for $R_f = 330 \text{ k}\Omega$ 7 CO2 K3



- d. Design a 3 input Summing Amplifier using OP-Amp Write the equations with suitable diagram. 8 CO2 K4

- 4.a. Design the Full adder using NOR gates only. 7 CO3 K3

- b. Design logic gate for Binary to BCD code Converter 8 CO3 K4

(OR)

c.	Express the Boolean function $F = xy + x'z$ in a product of Maxterm form	7	CO3	K4
d.	Realize the following function of four variables with 8:1 MUX. $F(A, B, C, D) = \sum (0,1,3,5,7,11,13,15)$	8	CO3	K3
5.a.	Explain about Master Slave J-K flip-flop and its operation with suitable diagram.	7	CO4	K3
b.	Convert and draw the logic gate for the conversion of S-R to J-K Flip Flop (OR)	8	CO4	K4
c.	Design a shift right SISO register using D Flip Flops. Show how a pulse 0101 is shifted using this type of register	7	CO4	K4
d.	Design a synchronous Mod-12 up counter.	8	CO4	K3

--- End of Paper ---