



GIET UNIVERSITY, GUNUPUR - 765022

B. Tech (Fourth Semester Regular) Examinations, May - 2024 21BECPC24001 - Digital Electronics (ECE)

Time: 3 Hours

Maximum: 70 Marks

(The figures in the right-hand margin indicate marks)

PART – A

(2 × 5 = 10 Marks)

Q.1. Answer **ALL** questions.

- | | CO # | Blooms Level |
|---|------|--------------|
| a. Find the radix of the number system where $24 + 17 = 40$. | CO1 | K1 |
| b. Show that the dual of the exclusive-OR is equal to its complement. | CO1 | K1 |
| c. Convert the following expression into a standard product of sums.
$Y = A(A + B + C)$ | CO2 | K2 |
| d. Write a characteristic equation and excitation table for the T flip-flop. | CO3 | K1 |
| e. How many $16K \times 1$ RAMs are required to obtain a memory with a word capacity of 64K? The word length is eight bits. | CO4 | K3 |

PART – B

(15 × 4 = 60 Marks)

Answer ALL questions.

- | | Marks | CO # | Blooms Level |
|---|-------|------|--------------|
| 2.a. Carry out the following additions:
(i) (+13, -11) using 1's complement notation.
(ii) (-15, +9) using 2's complement notation. | 8 | CO1 | K3 |
| b. Simplify the following Boolean functions to a minimum number of literals.
(i) $x(x' + y)$
(ii) $xy + x'z + yz$ | 7 | CO1 | K3 |
| (OR) | | | |
| c. Construct logic circuit using AND, OR, and NOT gate for the following Boolean function:
(i) $Y = (A + B)(A' + B')$
(ii) $Y = (A + B)(C' + D')(A' + C)$ | 8 | CO2 | K3 |
| d. In a tabular form, write the "2421" code and "Excess-3" code of decimal digit "0 to 9". What are the special properties of these codes? | 7 | CO1 | K2 |
| 3.a. Simplify the following Boolean function using a four-variable K-map:
$F(A, B, C, D) = \sum(0, 1, 3, 4, 5, 7, 9, 11, 15)$
and then, realize the simplified functions using logic gates. | 10 | CO2 | K3 |
| b. Reduce the Boolean expression $A + B[AC + (B + \bar{C})D]$ | 5 | CO1 | K3 |
| (OR) | | | |
| c. What is a full adder circuit? Draw its truth table. Design a full adder circuit using two half adder circuits and an 'OR' gate. | 10 | CO2 | K3 |
| d. Implement the following Boolean function with a multiplexer.
$F(A, B, C, D) = \sum(1, 3, 4, 11, 12, 13, 14, 15)$ | 5 | CO2 | K3 |
| 4.a. A magnitude comparator is a combinational circuit that compares two numbers A and B , and determines their relative magnitudes. The outcome of | 8 | CO2 | K3 |

the comparison is specified by three binary variables that indicate whether $A > B$, $A = B$ or $A < B$. Determine the algorithm to implement this comparator and draw a 2-bit magnitude comparator using the combinational circuit.

- b. Construct the 3×8 decoder using 2×4 decoders. 7 CO2 K3

(OR)

- c. What is the race-around condition? How is it eliminated in a master-slave JK flip-flop? 8 CO3 K2


- d. Explain how a $J-K$ can be constructed using D flip-flop. 7 CO3 K3

- 5.a. Design of a synchronous Mod-6 counter using JK flip-flops. 10 CO3 K3

- b. What is a shift register? Explain the principle of a 4-bit serial-in, parallel-out, shift register. 5 CO3 K2

(OR)

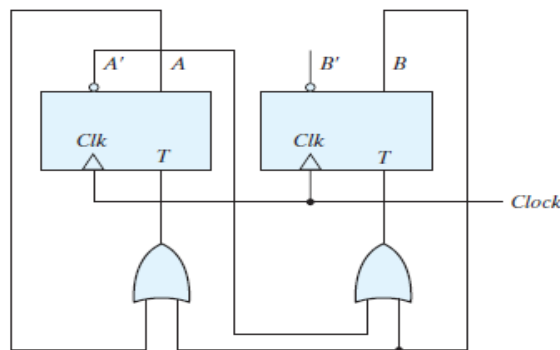- c. Derive the state table and the state diagram of the sequential circuit shown in the figure. 10 CO3 K3



- d. Design a combinational circuit using a ROM. The circuit accepts a 3-bit binary number and generates an output binary number equal to the square of the input number. 5 CO4 K3

--- End of Paper ---