

**GIET UNIVERSITY, GUNUPUR – 765022**

B. Tech (Fifth Semester Regular) Examinations, December – 2023

**21BELPC35001 – Power Electronics**

(EE &amp; EEE)

Time: 3 hrs

Maximum: 70 Marks


**Answer all questions****(The figures in the right hand margin indicate marks)****PART – A****(2 x 5 = 10 Marks)**

Q.1. Answer <b>ALL</b> questions	CO #	Blooms Level
a. Power MOSFET is a voltage-controlled device. Why?	CO1	K3
b. What losses occur in a thyristor during working conditions?	CO1	K2
c. Find the average value of output current for a 1-phase HW diode rectifier with R load, having RMS output current = 100A.	CO3	K3
d. Can you provide examples of how a DC chopper can be used in motor speed control applications?	CO4	K4
e. A step up chopper has input voltage 110 V and output voltage 150 V. The value of duty cycle is ?	CO5	K3

**PART – B****(15 x 4 = 60 Marks)**

<u>Answer <b>ALL</b> questions</u>	Marks	CO #	Blooms Level
2. a. A single phase 230V, 1Kw heater is connected across 1 phase 230V, 50Hz supply through an SCR. For firing angle delay of 450 and 900, Calculate the power absorbed in the heater element.	7	CO1	K3
b. Explain the constructions and switches characteristics of power MOSFETs.	8	CO1	K2
(OR)			
c. Illustrate the working of cosine firing circuit with neat block diagram.	7	CO2	K3
d. Calculate the required parameters for snubber circuit to provide dv/dt protection to SCR used in single phase bridge converter. The SCR has maximum dv/dt capability of 60V/μsec. The input line-line voltage has a peak value of 425 volts and the source inductance is 0.2mH.	8	CO2	K3
3.a. Explain the operation of full wave-wave uncontrolled rectifier supplying R-load with neat waveforms. Derive an expression for the average output voltage.	7	CO3	K3
b. For the shown half-wave rectifier, the source is a sinusoid of 120V rms at a frequency of 60 Hz. The load resistor is 5 Ω. Determine (a) the average load	8	CO3	K3

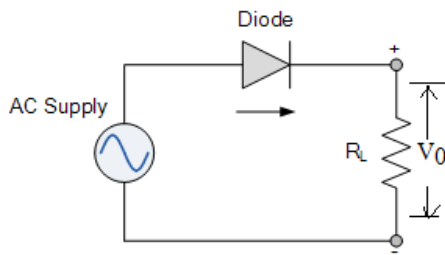current, (b) the dc and ac power absorbed by the load and (c) the power factor of the circuit.



(OR)

- |      |   |   |     |    |
|------|---|---|-----|----|
| c.   | Discuss the operation of single-phase half-wave diode rectifier with RL-load. Derive the average output voltage equation.                   | 7 | CO3 | K2 |
| d.   | Explain the operation of 3-phase diode bridge rectifier with resistive load. Draw the output voltage and current waveforms.                 | 8 | CO3 | K2 |
| 4.a. | A step-down dc chopper has input voltage of 230v with 10-ohm load, voltage drop across chopper is 2v, when it is on. For a duty cycle of 0. | 7 | CO4 | K3 |

Calculate (i) average and rms value of output voltage (ii) power delivered to the load

- |    |  |   |     |    |
|----|--|---|-----|----|
| b. | Is there any difference between the term's "boost" and "buck" converter? | 8 | CO4 | K3 |
|----|--|---|-----|----|

(OR)

- |      |   |   |     |    |
|------|---|---|-----|----|
| c.   | Discuss the operation of single-phase full wave rectifier with DC Motor-load. Derive the average and RMS output voltage equation.   | 7 | CO4 | K3 |
| d.   | Discuss the principle of operation of DC-DC step down chopper with suitable waveforms. Derive the expression for its average dc voltage.                                    | 8 | CO4 | 3  |
| 5.a. | The single-phase full bridge inverter has resistive load of $R=4$ ohm and dc Input voltage is 48v. Determine rms output voltage at the fundamental Frequency, output power. | 7 | CO5 | K4 |

- |    |  |   |     |    |
|----|--|---|-----|----|
| b. | Write the principle of operation of Cyclo-converter connected to R-Load. | 8 | CO6 | K3 |
|----|--|---|-----|----|

(OR)

- |    |   |   |     |    |
|----|---|---|-----|----|
| c. | How does a UPS (Uninterruptible Power Supply) work?   | 7 | CO6 | K3 |
| d. | The single-phase half bridge inverter has resistive load of $R=10$ ohm and dc input voltage is 220v. Determine rms output voltage, average value, RMS current and output power. | 8 | CO5 | K4 |

--- End of Paper ---